

Architectures & RF Circuits for Miniature Wireless Transceivers

Asad A. Abidi

**Electrical Engineering Department
University of California, Los Angeles**

(310) 825 9490 (Phn)

(310) 825 7028 (Fax)

abidi@icsl.ucla.edu



Outline

- ♦ ICs in Broadcast Radio Receivers
- ♦ ICs in Wireless Paging Receivers
- ♦ ICs in TV Tuners
- ♦ ICs in Cellular Telephone Transceivers
- ♦ ICs in Spread-Spectrum Wireless Transceivers
- ♦ ICs to Enable Future Transceivers


Examples of Miniature Radios

- ✓ Broadcast Receivers (FM at 100 MHz RF), such as the Walkman personal entertainment device
- ✓ Paging Receivers (150 MHz to 900 MHz RF) such as the Motorola Bravo
- ✓ GPS Receivers (2 GHz RF), such as the Sony Pyxis
- ✓ Cellular Telephone Transceiver Handsets (900 MHz RF) such as the Motorola MicroTac
- ✓ Wireless LAN Transceivers (900 MHz or 2 GHz RF), such as the Proxim or Plessey card

Early Preoccupations with ICs for Radio Receivers

- Potential of applying IC technology to radio receivers has occupied companies since mid-1960's
- Motorola's classic series of textbooks on IC design suggest these concerns:
 - "Integrated Circuit Design: Principles & Fabrication" (Warner & Fordemwalt, eds., 1965) discusses difficulty of making *spiral inductors* on silicon substrate.
 - "Analysis and Design of Integrated Circuits" (Meyer, Lynn, and Hamilton, eds., 1968) contains chapters on *tuned amplifiers* and *gyrator filters*
- Technology limits did not permit application of silicon ICs to RF sections until 1970s. Radios were built with discrete VHF/UHF bipolar transistors, FETs, and discrete passive components.

Dynamic Range in a Receiver

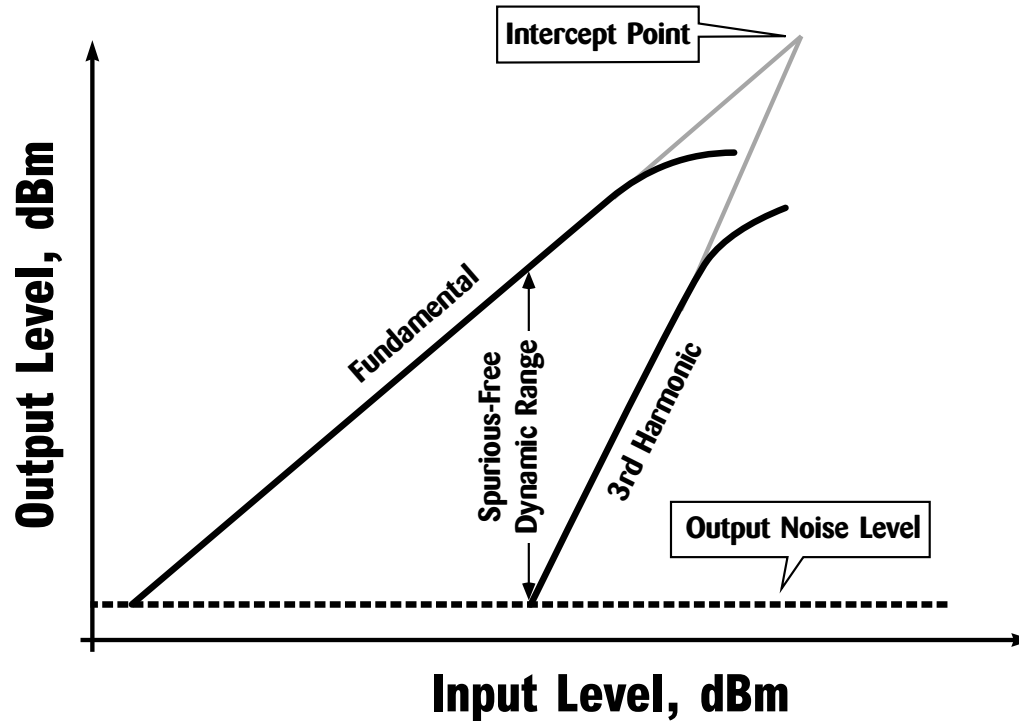

Early Uses of ICs in FM Receivers

📄 Peil, McFadyen, GE, 1977

- Integration of transistors in IF amplifier strip, FM demodulator and power amp. Off-chip inductors, capacitors, ceramic resonators.
- Leads to reduction in parts count, lowered power dissipation, and miniaturization.
- Some circuits only possible in monolithic IC form:

High gain, direct-coupled differential limiting amplifiers

Double-balanced (analog multiplier) mixers

On-chip AM front-end

Off-chip FM RF amplifier and mixer

7 off-chip tuned circuits

1.9-V operation


Thermal feedback on-chip

Coupling through on-chip
power supplies

Parasitic coupling between IC
pins at high frequencies

Frequency Allocation Plan Example

Siemens Wideband TV Tuner IC

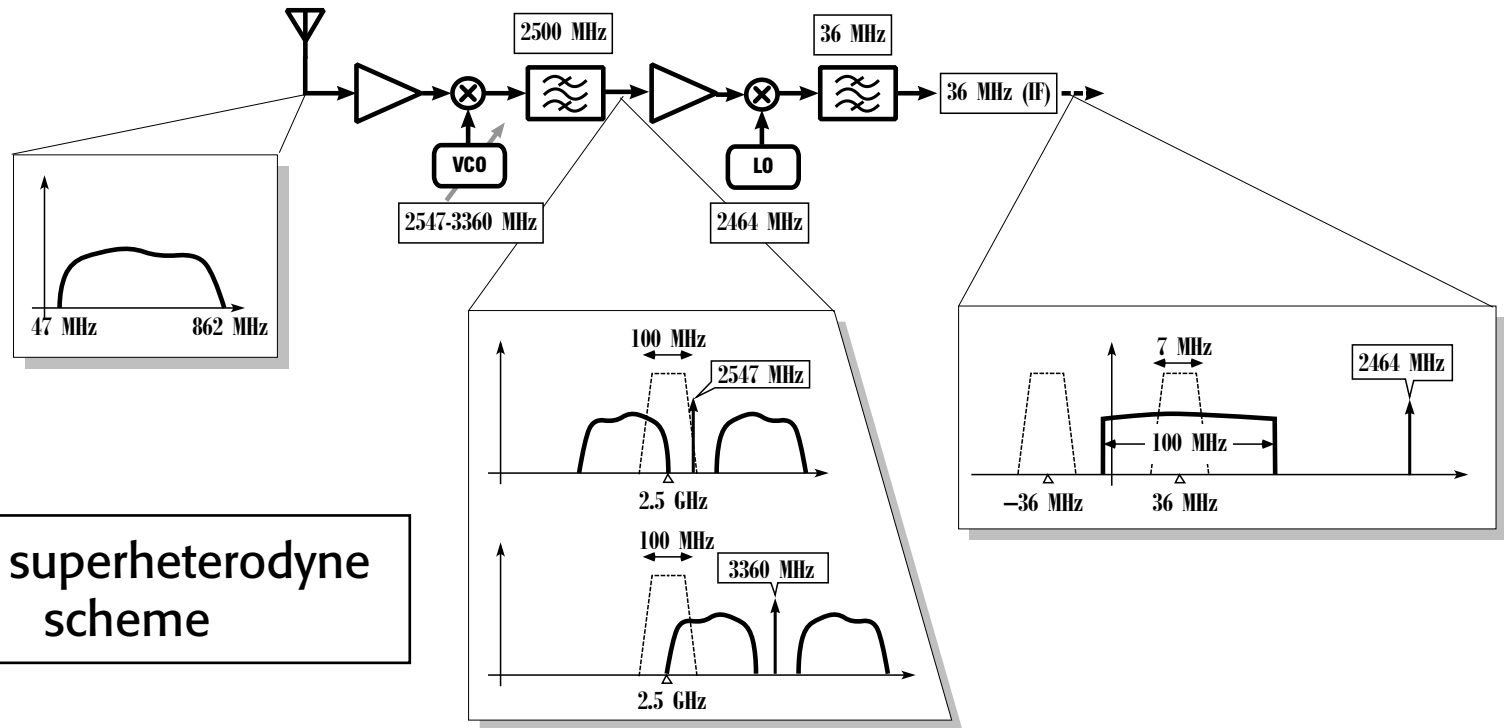



- One GaAs IC tunes all TV bands, from VHF to UHF
- Upconversion serves two functions:

Avoids *image frequency* reception, because antenna cannot tune 5 GHz

Reduces *fractional tuning* range of first VCO to cover entire TV band

Conventional FM Receiver Front-End


📖 Kanow, Siewert, Philips, 1981

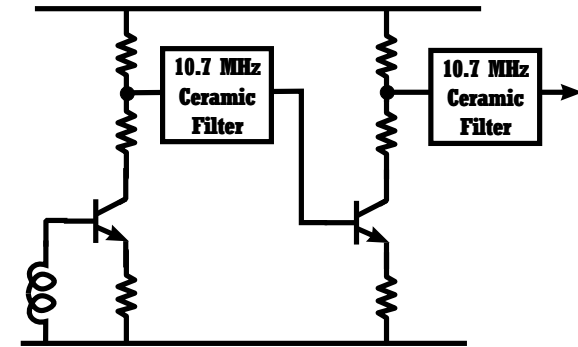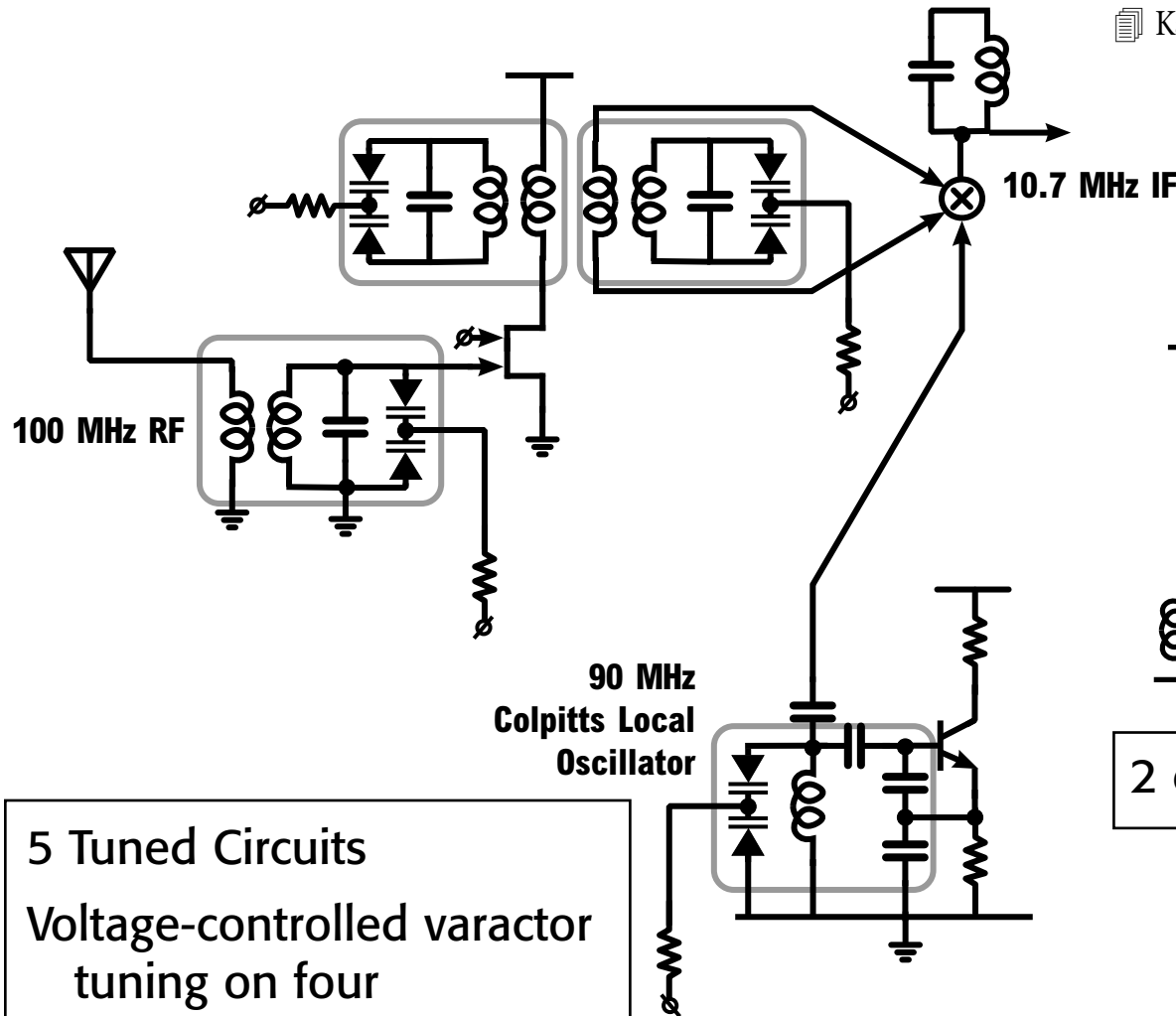

2 ceramic resonator filters

Keys to Greater Integration

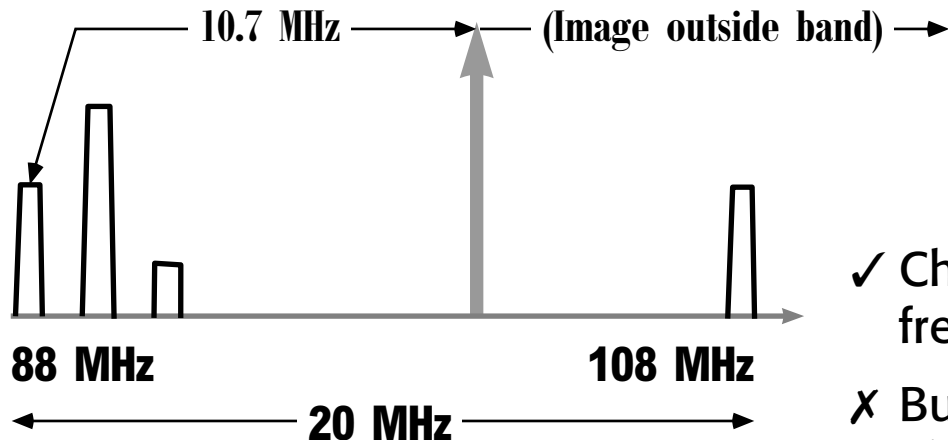- ➡ Reduce amount of RF filtering
- ➡ Reduce number of tuned components
- ➡ Bring RF amplifier on-chip (use off-chip tuned load if necessary)
- ➡ Filters for greater selectivity and image-rejection should be on-chip




- ✓ Choice of high IF suppresses image frequency
- ✗ But, difficult to make on-chip active filters, particularly with high dynamic range and low power. Need 10.7 MHz bandpass with 150 kHz passband


Low IF FM Receiver

☞ Kasperkovitz, Philips, 1981 & 1983

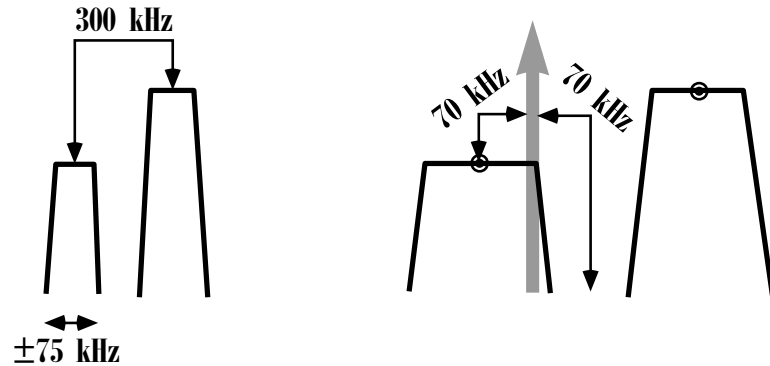☞ v. Dooremolen & Hufschmidt, Philips, 1983




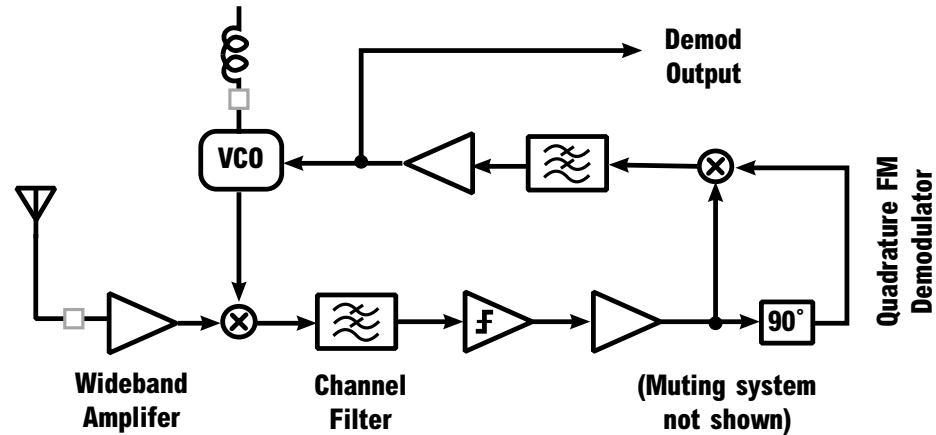- ✓ Lower the IF so that on-chip lowpass filters may define channel bandwidth
- ✗ Zero IF has no image, but cannot use limiting amplifier to remove AM noise
- ✓ 70 kHz IF means that image lies in inter-channel band; only contributes extra noise!



- Negative feedback in frequency-locked loop compresses FM swing to ± 15 kHz
- First LPF acts as channel filter; 4th order active-RC implementation with 100 kHz cutoff frequency
- 15 capacitors, 2 inductors, 8 mA drain from 4.5V


Single-Chip FM Radio

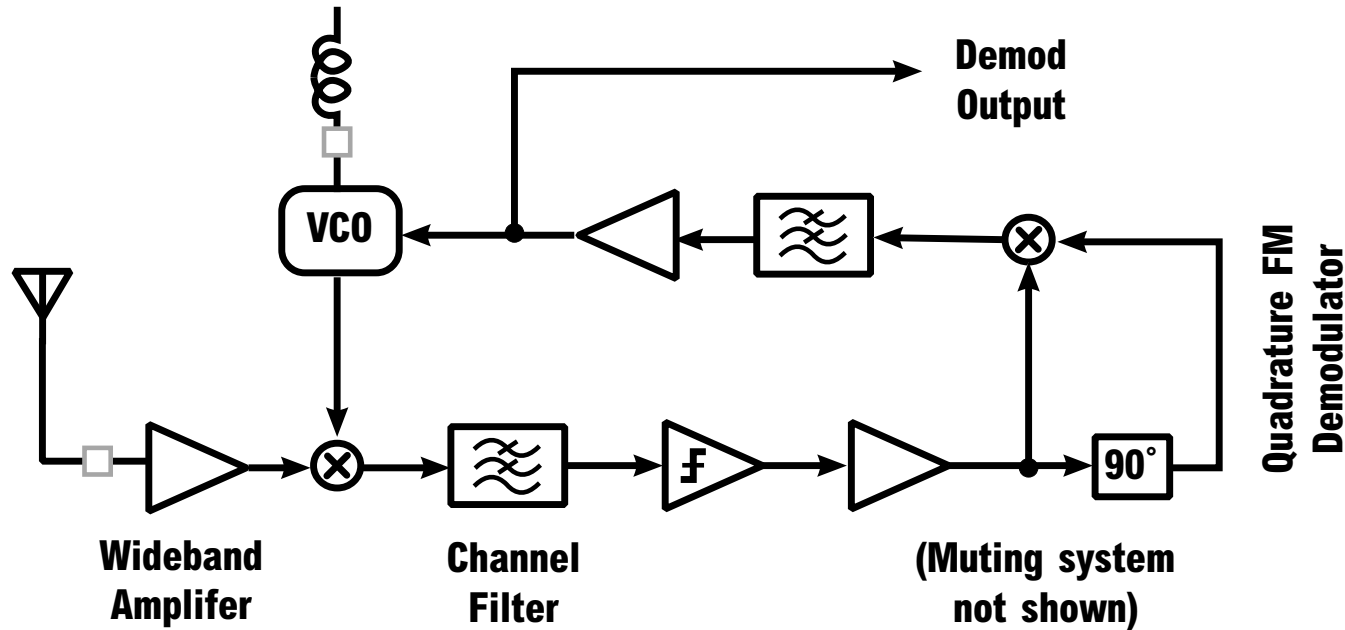

- Negative feedback in frequency-locked loop compresses FM swing to ± 15 kHz
- First LPF acts as channel filter; 4th order active-RC implementation with 100 kHz cutoff frequency
- 15 capacitors, 2 inductors, 8 mA drain from 4.5V




The Image-Cancellation Mixer

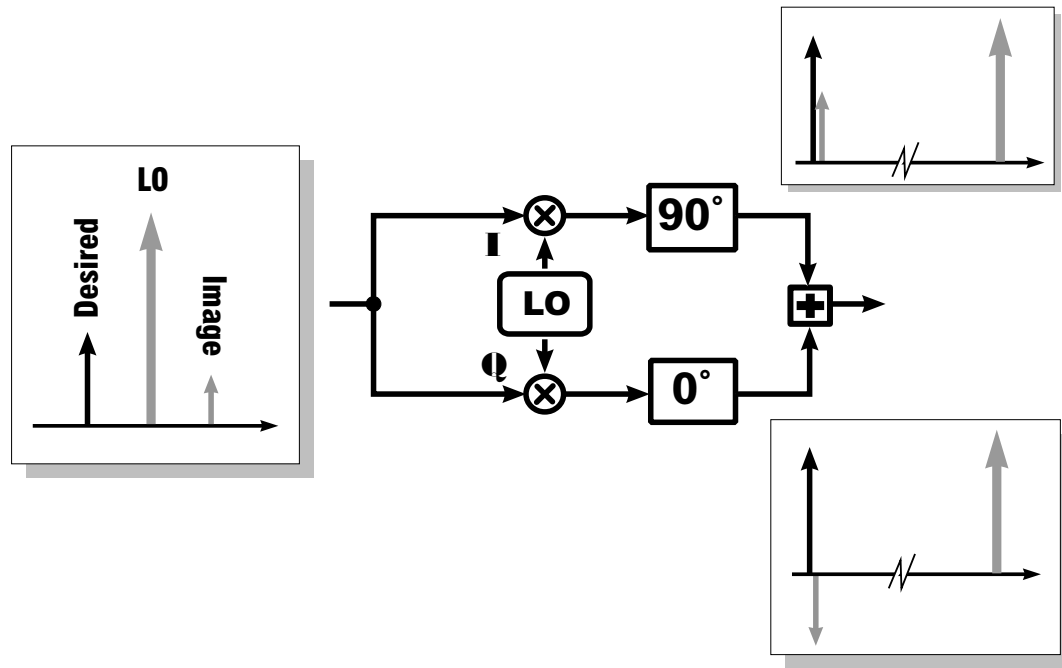

- Complex mixing eliminates need for image-cancellation filter
- Image suppression depends on exactness of quadrature; 1° error gives about 40 dB suppression
- Phase-shift in IF path usually obtained with delays or allpass filters
- Quadrature LO outputs from $\div 2$, $RC-CR$ network, or inherently from oscillator

Alternative Single-Chip FM Receiver


Okano, *et al.*, Sony, 1992

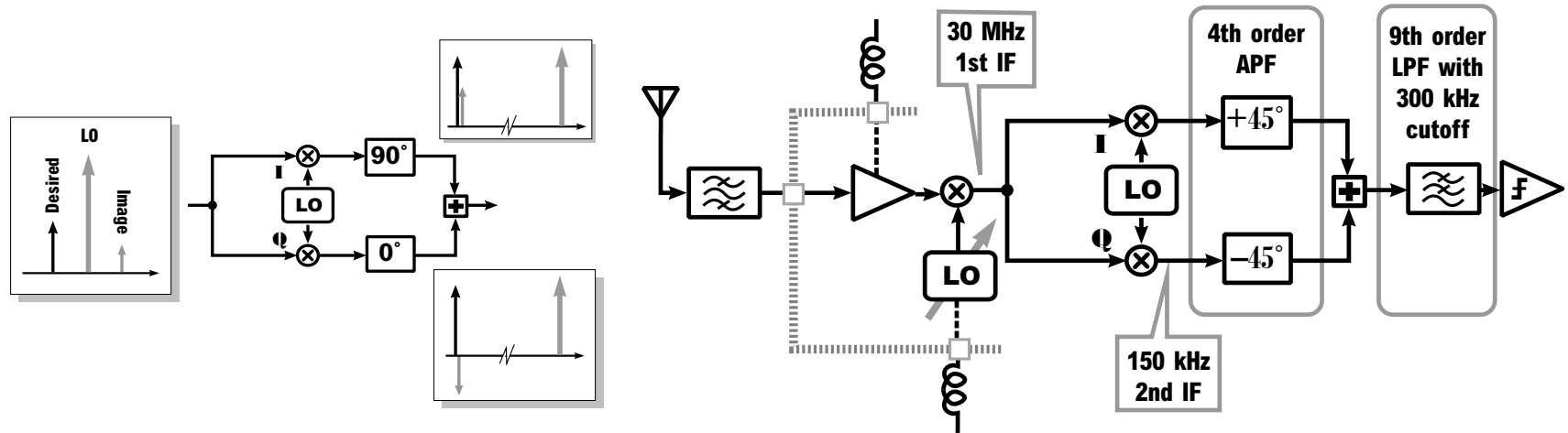

- Complex mixing eliminates need for image-cancellation filter
- Image suppression depends on exactness of quadrature; 1° error gives about 40 dB suppression
- High IF affords better image rejection
- Single off-chip BPF covering entire FM band
- Image-rejection mixer suppresses unintended channel captured by 150 kHz second IF
- Channel filter and phase-shift networks are on-chip active-RC


Circuits for Low-Voltage Operation

RF Amplifier and First Mixer

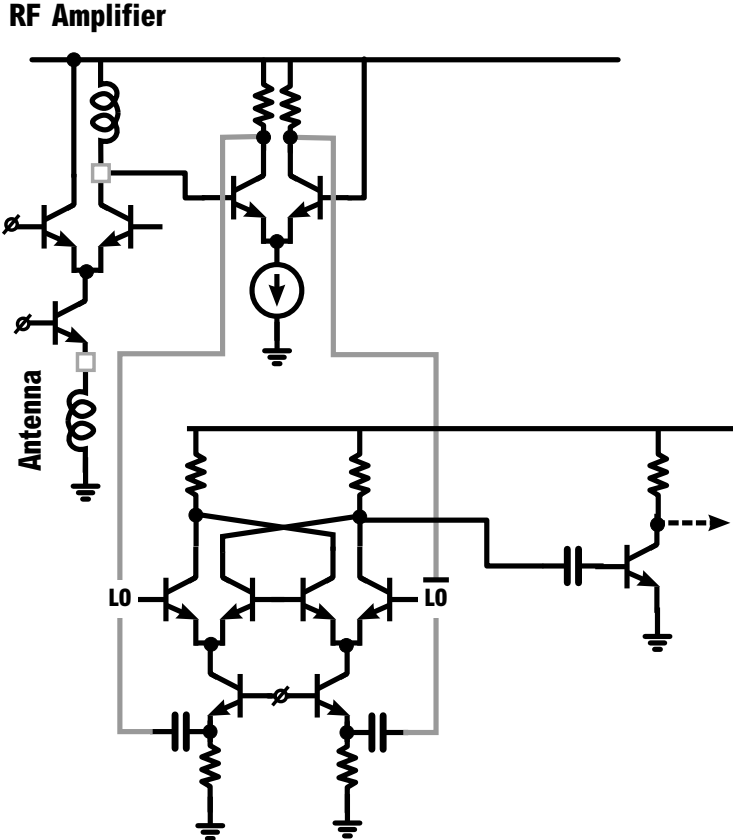


0.9V to 4.5V operation


Second Mixer

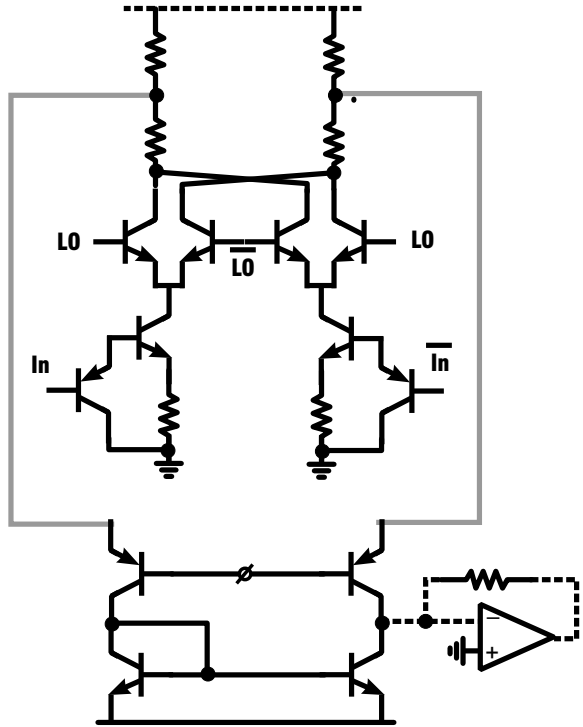

Local Oscillator

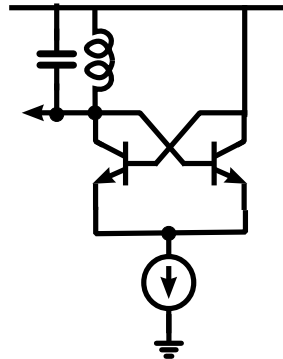


Performance of Low-Voltage Receiver

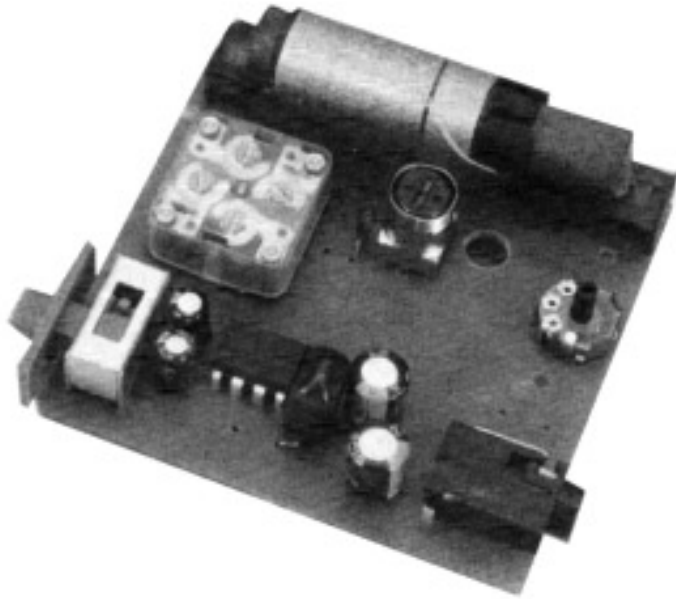

Current Drain	16 mA
FM Selectivity	40 dB at 400 kHz
Image Rejection	39 dB
FM Max SNR	60 dB
Sensitivity for quieting	10 μ V
THD	0.1%

DBS TV Receivers

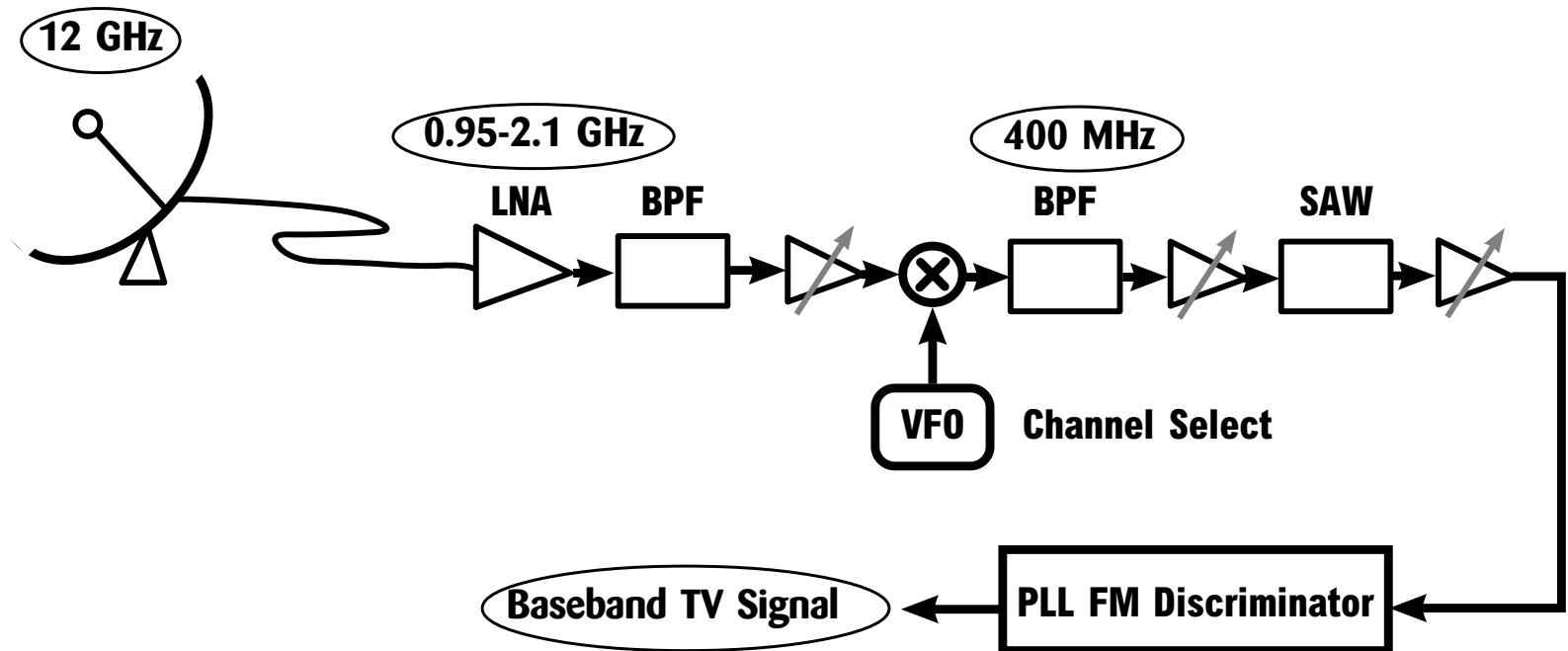

Transmission at 12 GHz

Conversion to first IF (900 MHz to 2 GHz) in receiver antenna

ICs have been developed for first IF onwards -- miniature DBS receivers in TV sets and VCRs



Front-End RF Amplifiers



Yamamoto, *et al.*, *IEEE Trans. on CE*, Aug. 1989



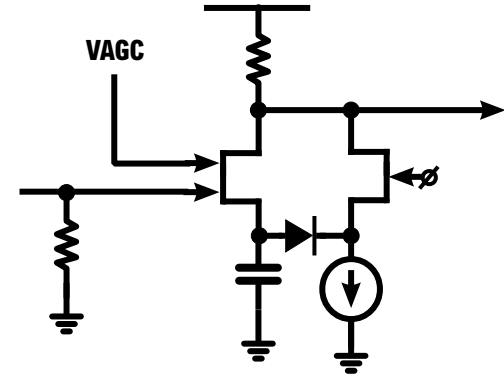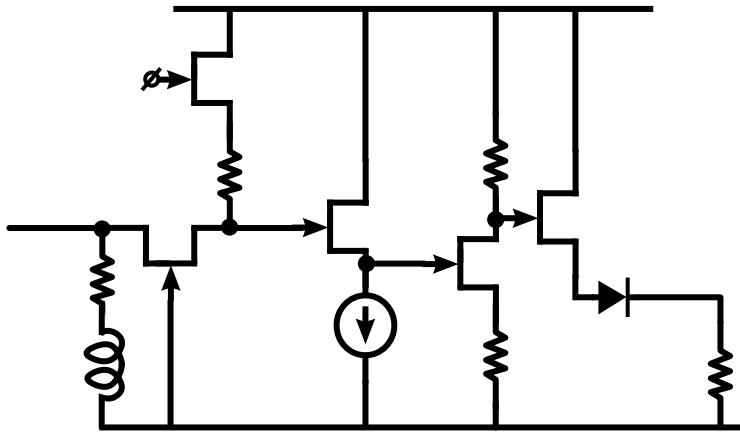Yamamoto, *et al.*, *IEEE Trans. on CE*, Aug. 1992



Gain	> 9 dB
Noise Figure	8 dB
Input VSWR	< 2
3rd-order IM	< -58 dBc at max input
Reverse isolation	> 25 dB
Power dissipation	120 mW from 5 V
Technology	1- μ m MESFET

Receive more than 20 DBS channels, with more than 50 dB dynamic range

Radio Paging Receivers



- Importance of paging people on the move with miniature radio receivers recognized in the late 1950's
- Bellboy Trials at AT&T in early 1960's. Local area paging by FM of 150 MHz with three tone set. Receiver contains vibrating reeds tuned to recognize its own code.
- Small size and long battery life recognized as keys to success
- Modern pagers use digital signalling at 500 b/s
- Paging receivers are perhaps the most highly evolved, widely used RF device. High functionality / unit volume, long battery life.

Features of the Bellboy Receiver


- Operates on 4-V supply
- Uses ten transistors in entire receiver
- Single-conversion superheterodyne with 6 kHz IF
 - Circuits operate at low currents
 - Capacitively-coupled 10 kHz lowpass filter for channel selection

📄 Mitchell & van Wynen, Bell Labs, 1961

📄 Kerwein & Steiff, Bell Labs, 1963

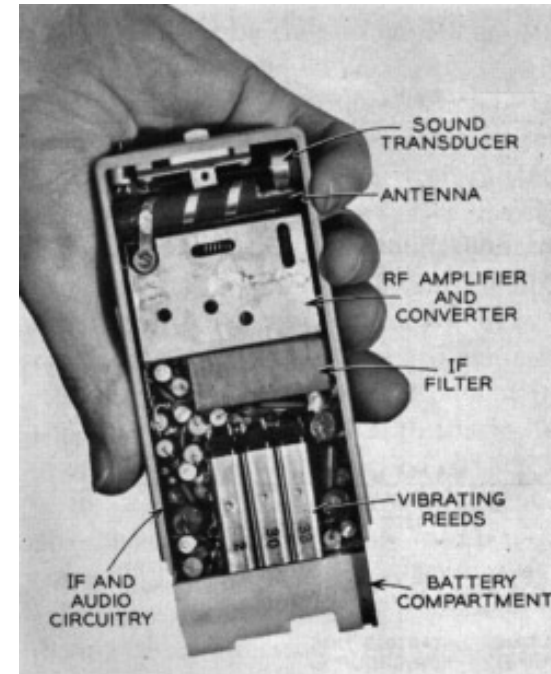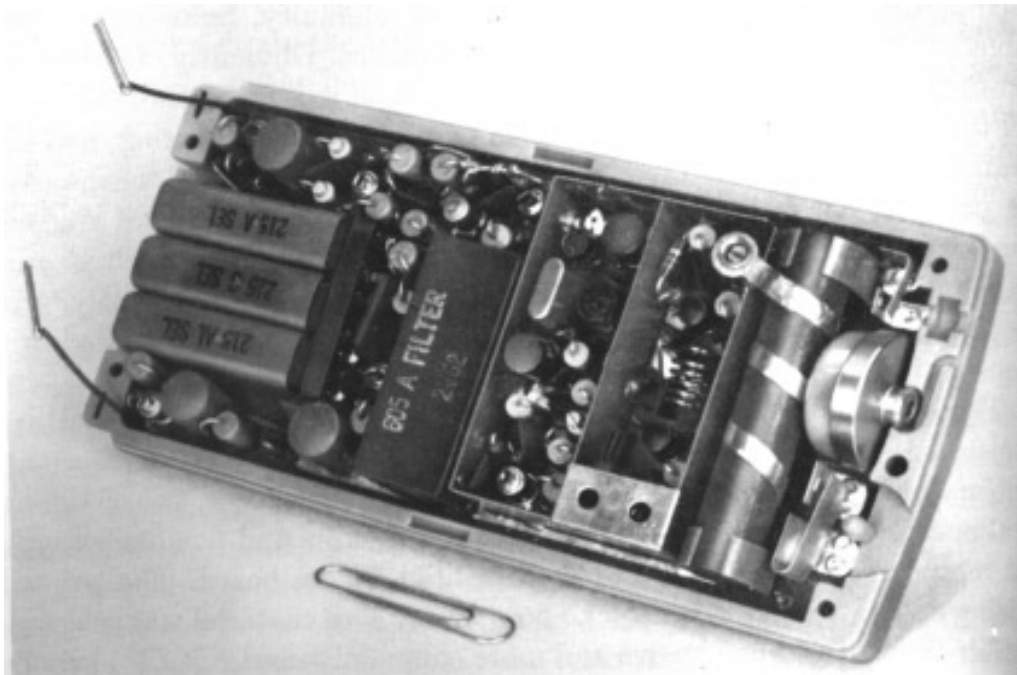


Digital Pager Signalling

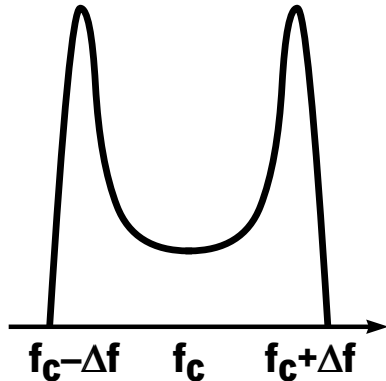

- POCSAG signalling standards used
 - RF is 150 MHz in Japan, 450 MHz to 900 MHz in US and Europe
 - Binary FSK suppressed-carrier spectrum contains information at ± 4.5 kHz around center frequency
-
- Early paging receivers used conventional double-superheterodyne architectures, off-chip bandpass filters, and a frequency discriminator to detect the two tones. Too complex.
 - Solution was required to radically simplify the receiver by exploiting the features of the signalling


Direct Conversion Reception

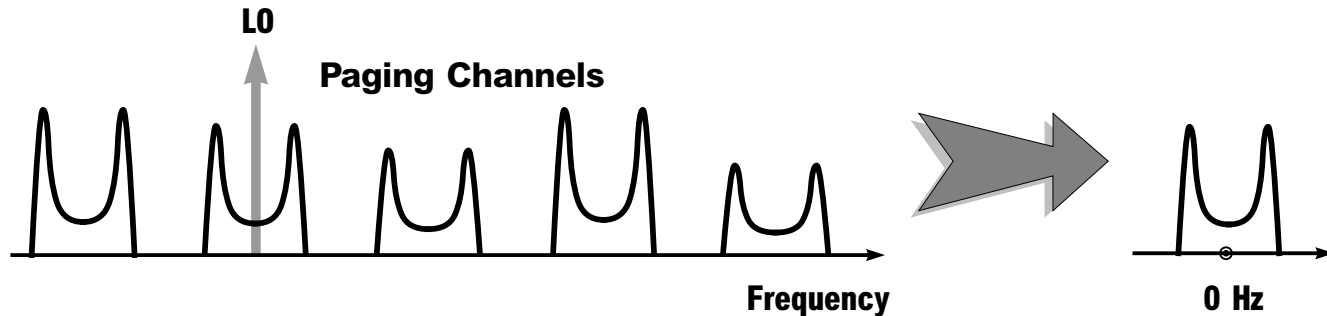

- Zero IF is the simplest possible receiver
 - ✓ Lowpass channel filters only
 - ✓ Minimum processing at high frequencies
 - ✓ No image response to worry about!
- Potential problems of Zero IF
 - ✗ DC and flicker noise add to converted signal
 - ✗ Local oscillator (at RF) can leak out of antenna

Direct Conversion Paging Receiver


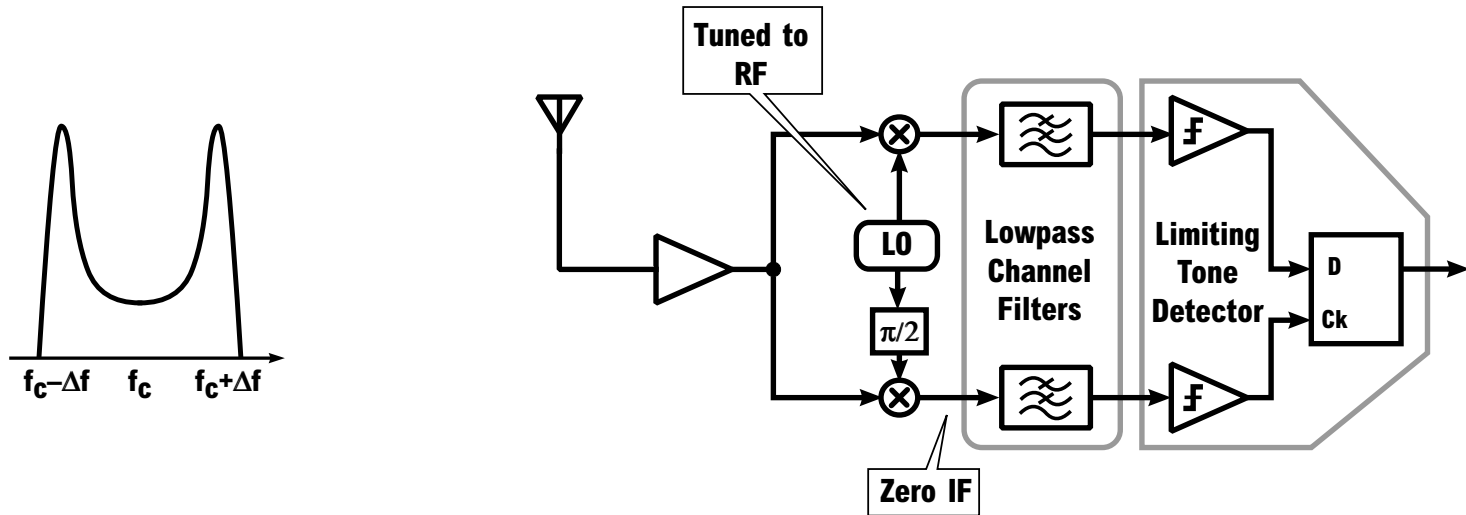
 Vance, ITT Standard Telecommunications Labs, 1980, 1982



- Extremely simple receiver
- Very simple detector in principle; only a flip-flop!
- RF amp and LO are the only high frequency blocks on chip
- AC coupling eliminates DC offsets; seek energy only at ± 4.5 kHz
- Naturally suggests a single-chip implementation!

Paging Receiver Prototype

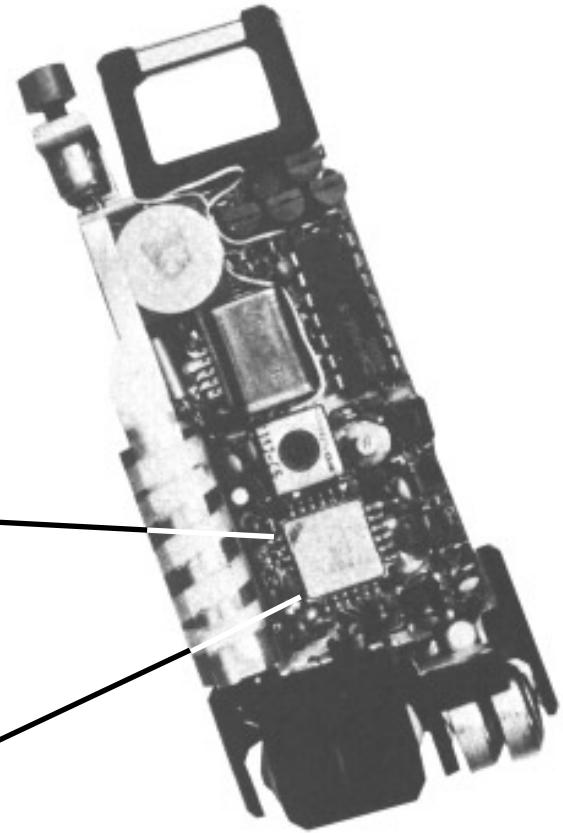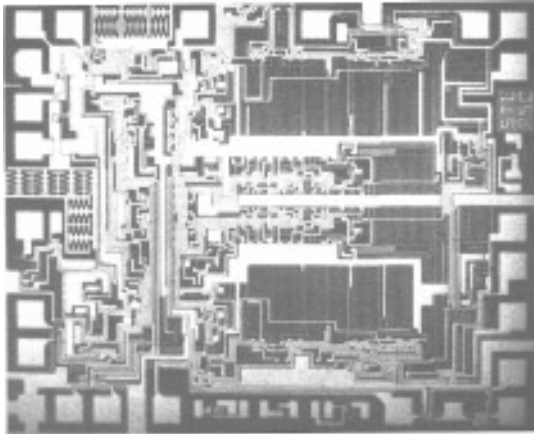
- Si Bipolar receiver IC drains 2.5 mA from 1.8 V in active mode (lowered to 50 μ A in standby)
- Off-chip capacitors required for AC coupling of IF signal, and for channel lowpass filters




Single-Chip Paging Receivers

- Two-chip pagers are now standard. One IC for receiver, one for user interface.
- Only off-chip components are inductor load for RF tuned amplifier, quadrature phase-shift network, and crystal
- Low-frequency active filters (e.g 7th order lowpass filter with 15 kHz cutoff) require large on-chip capacitance

 Burt, GEC-Plessey, 1992

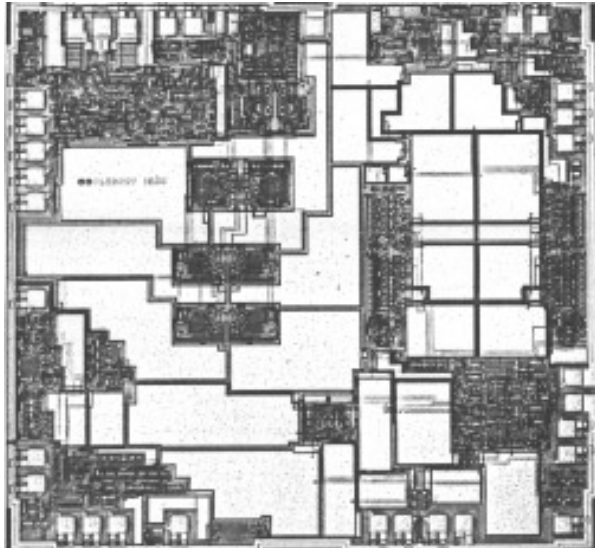


 Wilson, Philips, 1991

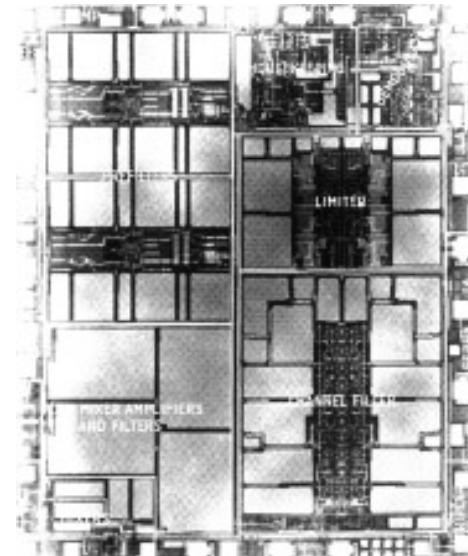

Cellular Telephones

- The first widespread *two-way* wireless communications devices
- Success in the market depends on small volume handset, long battery life
 - ⇒ Integration is the key!
- Most cellular telephones today are double superheterodyne transceivers, receiving and transmitting in separate frequency bands
- High frequency ICs used therein are building blocks. Relatively small levels of integration in RF portions.


Analog FM Cellular Phone Front-End

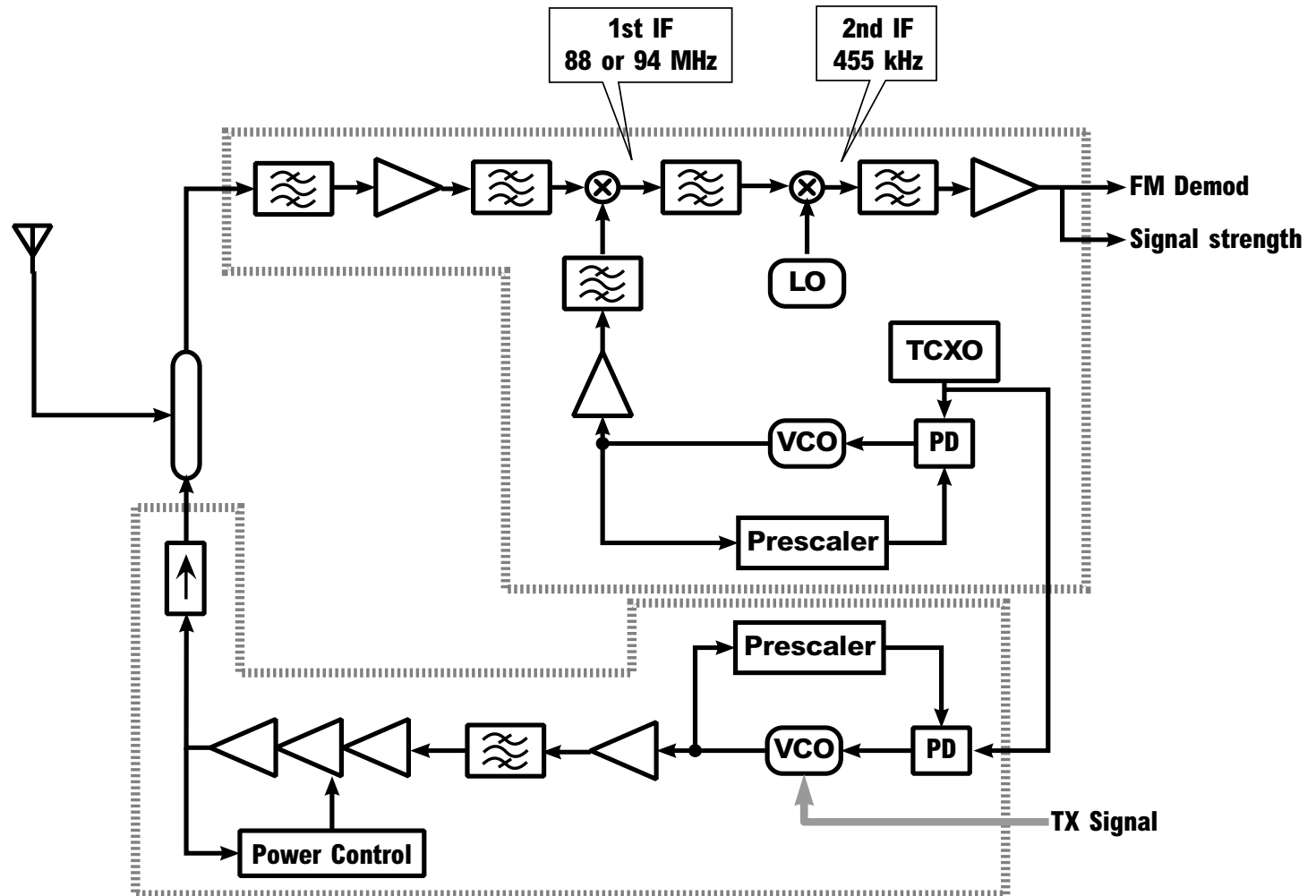



IF ICs in Cellular Telephones

- Medium-scale integration used in 100 MHz first IF blocks (typically silicon bipolar)

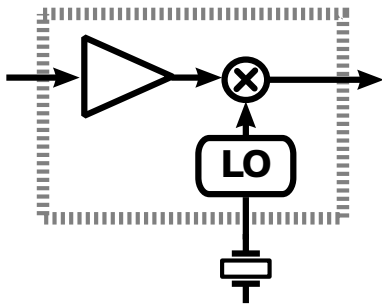Include mixers, IF amplifier chain, signal strength indicators



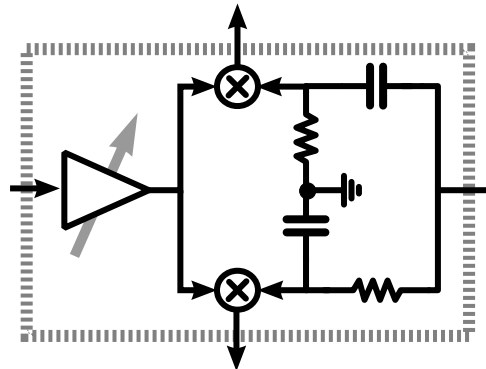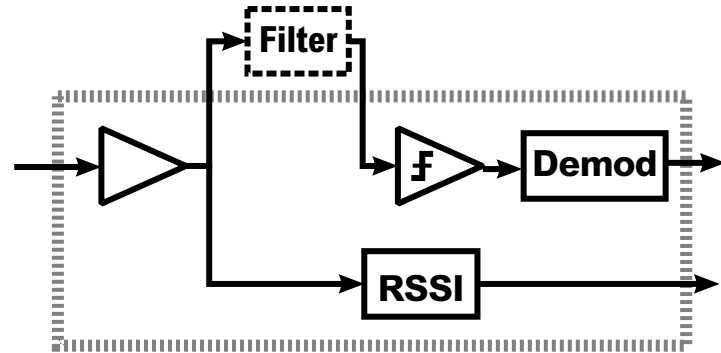Anderson & Zavrel,
Philips/Sigmetics, 1985



Koullias, *et al.*, AT&T, 1990



RF ICs in Cellular Telephones

- Small-scale integration, predominantly as GaAs MESFET ICs, for operation at 900 MHz to 2 GHz. This is the “low-end” of the economically feasible frequency range for this technology.
- Effort in recent years to reduce current drain of these ICs, and to increase power conversion efficiency
- Scaled discrete transistors in miniature packages continue to compete, although at disadvantage of higher assembly costs



Typical SSI RF-ICs **LNA (Low Noise Amplifier) ICs**
LNA-Mixer Pairs
Power Amplifier Modules

GaAs ICs for Receiver Front End

Imai, *et al.*, NTT, 1991

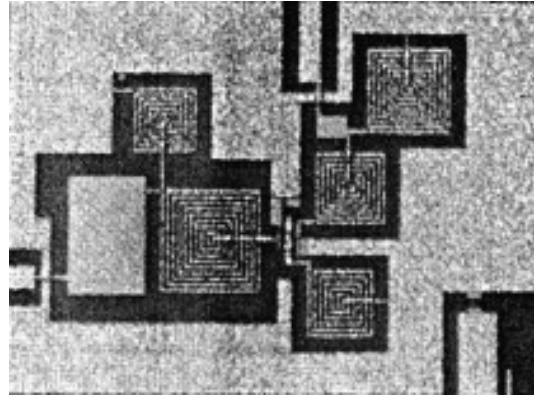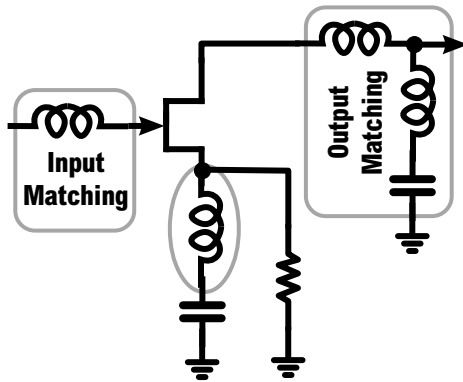


Gain	11.5-13 dB
Noise Figure	2.5-3 dB
3rd-order IM	-60 dBc at -30 dBm input
Frequency Band	1.5-1.7 GHz
Power dissipation	10 mW from 3 V
Technology	0.3- μ m SA MESFET

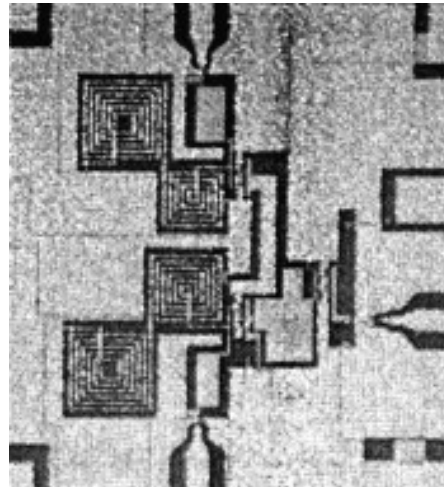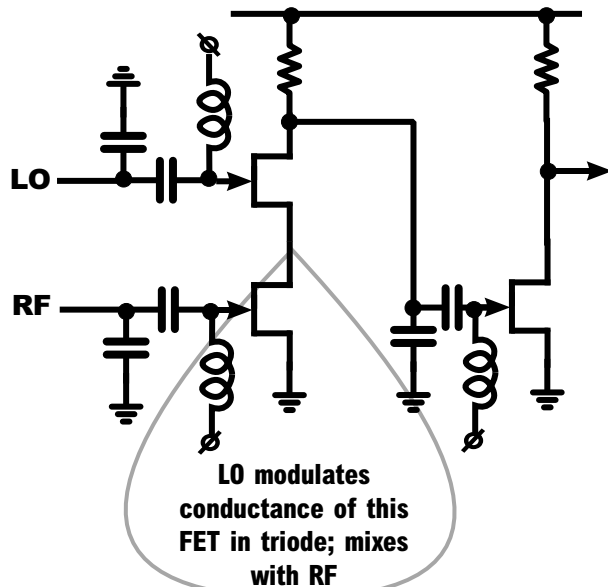

Conversion Gain	12.5 dB
Noise Figure	12.6 dB
Intercept Point	-7 dBm
Frequency Band	1.5-1.7 GHz
Power Dissipation	10 mW from 3-V
Technology	0.3- μ m SA MESFET





GaAs ICs for Transceiver

📄 Sakai, *et al.*, Matsushita, 1992

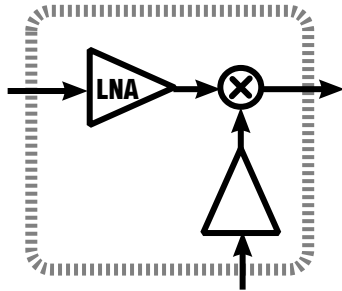

Amplifier


Mixer

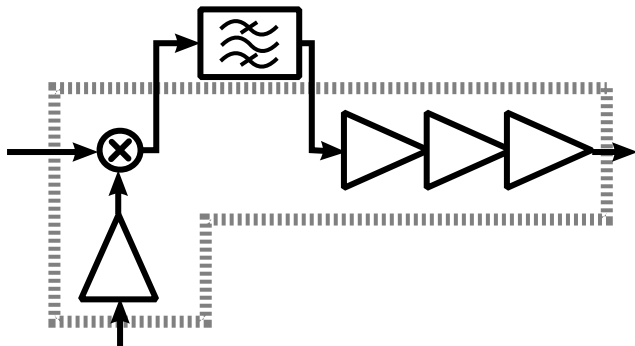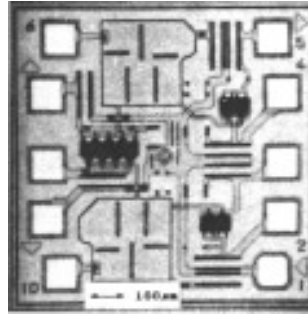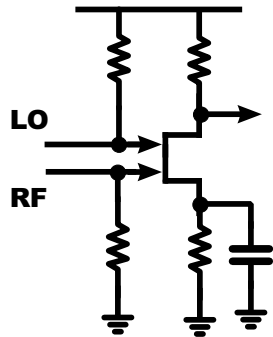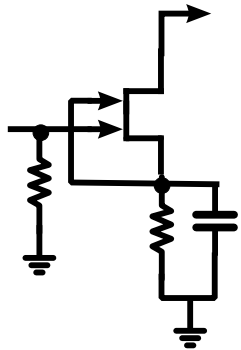


Gain	21 dB
Noise Figure	3.5 dB
3rd-order IM	-30 dBc at -30 dBm input
Frequency Band	0.9 GHz
Power dissipation	15 mW from 3 V
Technology	1-μm Dual-Gate MESFET


Conversion Gain	13 dB
Spurious Level	-80 dBc
Frequency Band	0.9 GHz
Power dissipation	27 mA from 3 V
Technology	1-μm Dual-Gate MESFET


GaAs ICs for Receiver Front-Ends

 Hara, *et al.*, Sharp, 1993

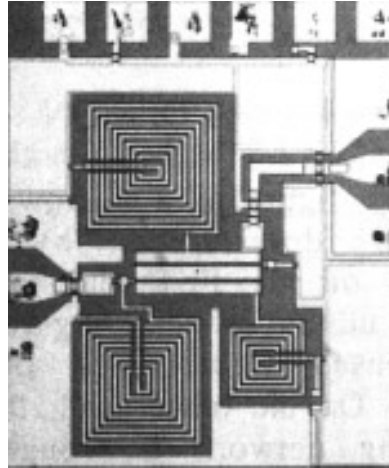

Gain	15 to 3 dB (controllable)
Noise Figure	3 dB
3rd-order Intercept	6.5 dBm
Frequency Band	1.5-1.7 GHz
Power dissipation	1.8 mA from 3 V
Technology	0.6- μ m MESFET


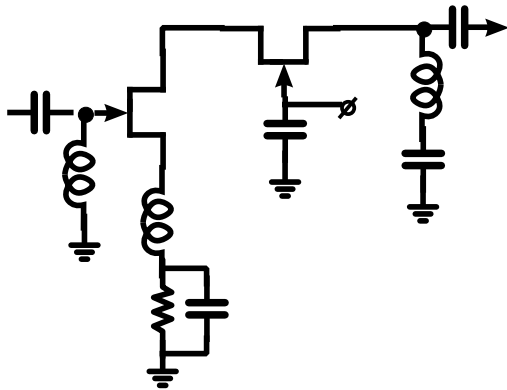


 Kermarrec, *et al.*, M/A-Com, 1992



Gain	14.5 dB
Noise Figure	1.7 dB
3rd-order IM	-55 dBc at -30 dBm input
Frequency Band	1.9 GHz
Power dissipation	3.2 mA from 4 V
Technology	1- μ m E/D MESFET

GaAs ICs for Receiver Front-Ends

Ohgihara, *et al.*, Sony, 1993

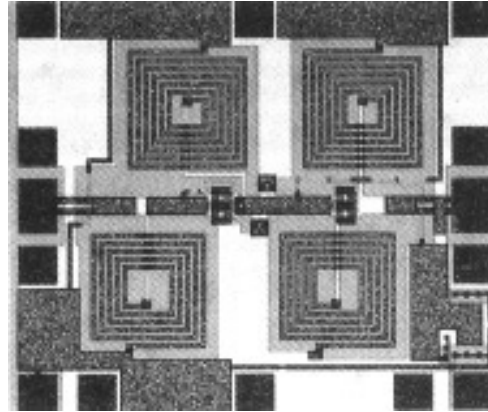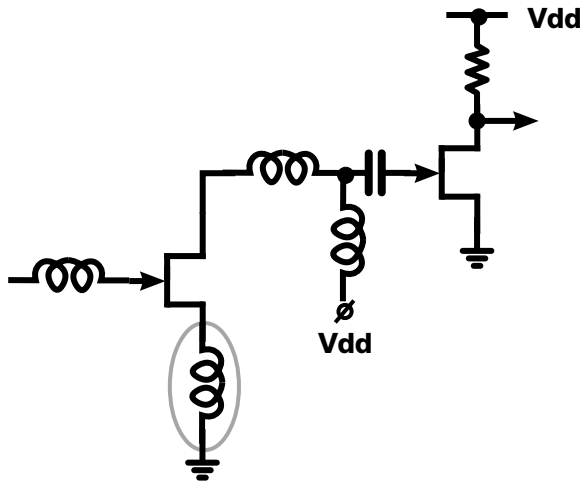

Gain	18 dB
Noise Figure	2.8 dB
Intercept Point	7 dBm (output)
Frequency Band	2 GHz
Reverse Isolation	21 dB
Power Dissipation	4 mA from 3 V
Technology	0.5- μ m GaAs JFET

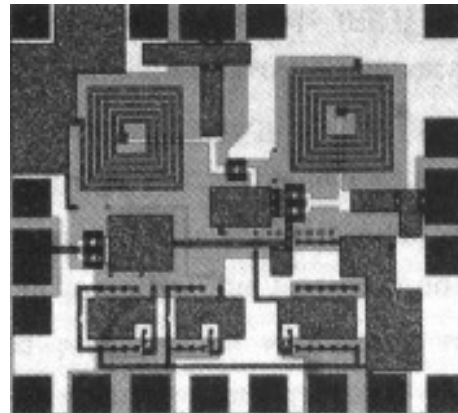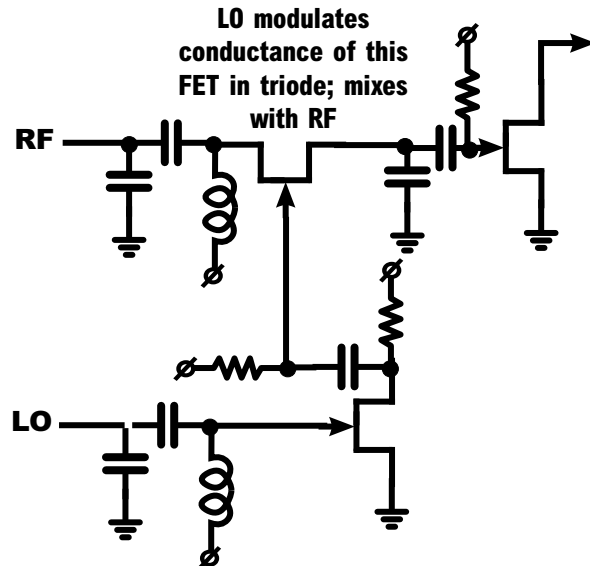


Conversion Gain	5.7 dB
Noise Figure	10.8 dB
Intercept Point	8 dBm (output)
Frequency Band	2 GHz
LO-RF Isolation	13 dB
Power Dissipation	4 mA from 3 V
Technology	0.5- μ m GaAs JFET

Key Components in Cellular Telephone


Upconversion Mixer

Woo, *et al.*, Pacific Monolithics, 1992

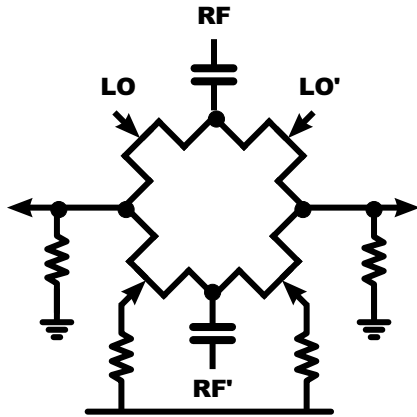


Transmitter VCO

Beyer & Lipperer, Siemens, 1992

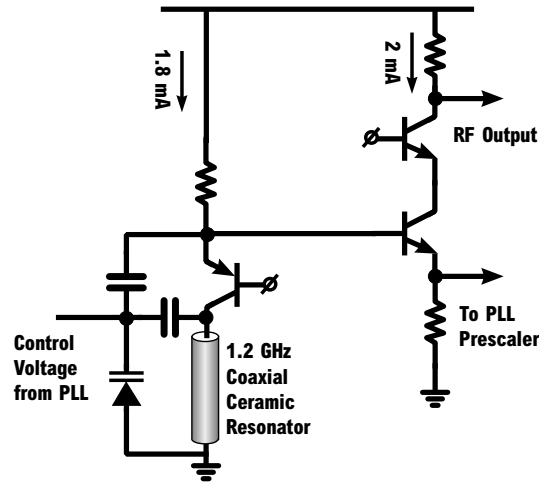

- VCO usually discrete, tuned by ceramic resonator for high Q \Rightarrow low phase noise
- Varactor adjusts oscillation frequency


Power Amplifier

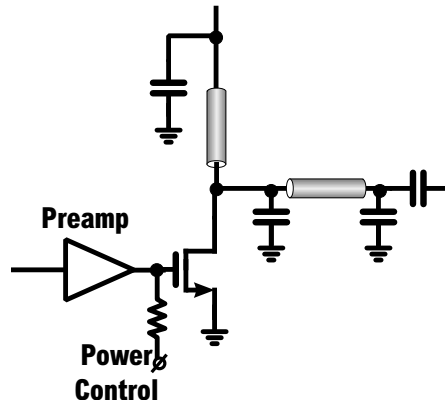


- Almost always a separate module with heat-sink package
- Designed for high power conversion efficiency
- Class-C operation, followed by impedance-matching circuits and filter to remove harmonics
- Typically a cascade of single FET stages, appropriately biased


Power Amplifier

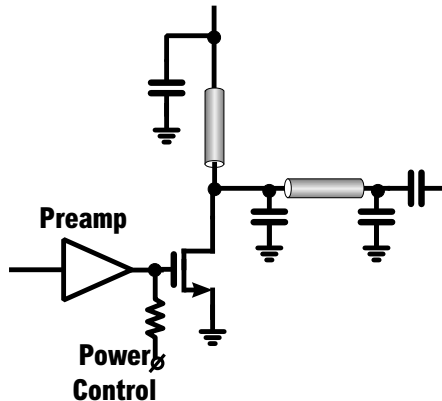- Almost always a separate GaAs module with heat-sink package
- Designed for high power conversion efficiency
- Class-C operation, followed by impedance-matching circuits and filter to remove harmonics
- Typically a cascade of single FET stages, appropriately biased






Smaller Telephone Handsets

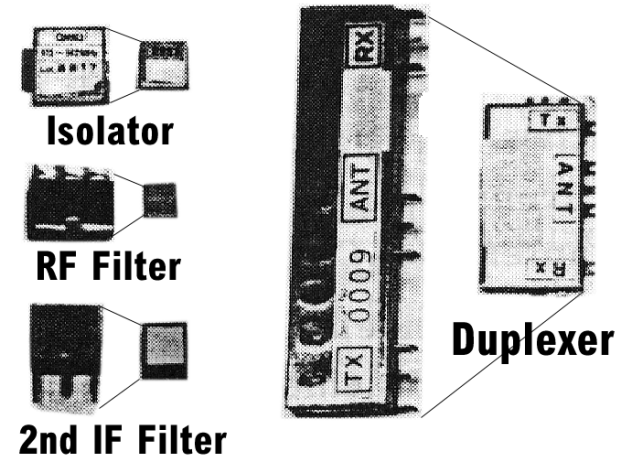


 Shimizu, *et al.*, NTT, 1991

- Handsets are attaining smallest practical size: 150 cc, 230 g, distance between human mouth and ear
- Miniaturization comes from reduction in size of *passive components* and their *packages*, not from greater integration of the electronics!

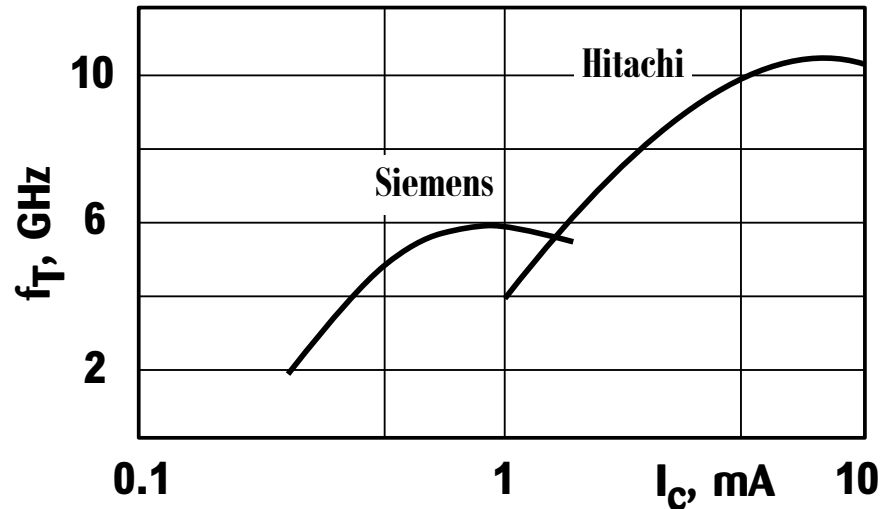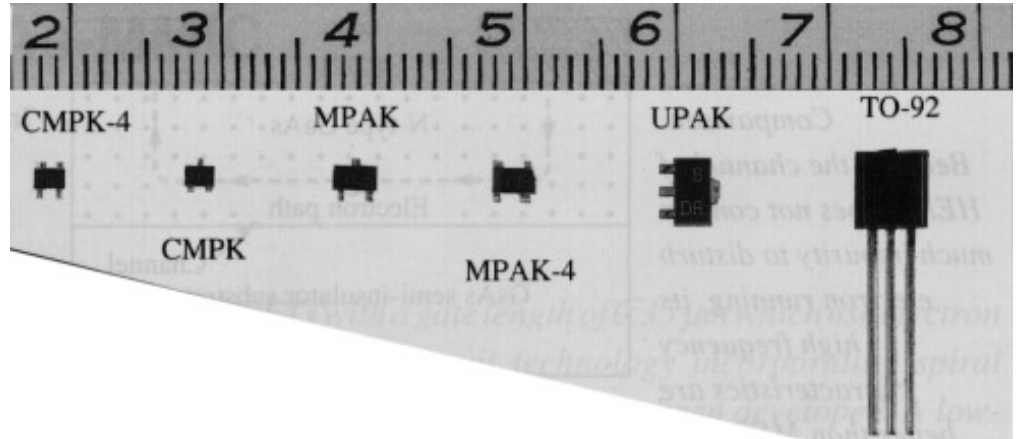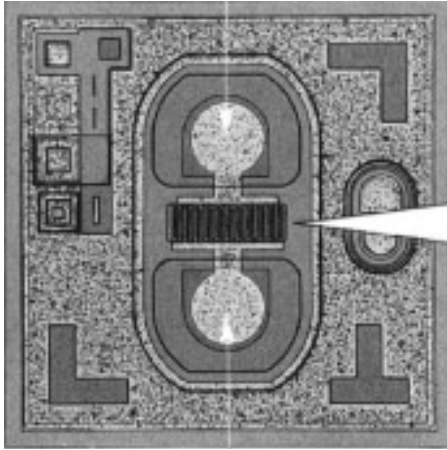Discrete Bipolar Transistors in Low-Power RF Applications




ICs in Television Tuners

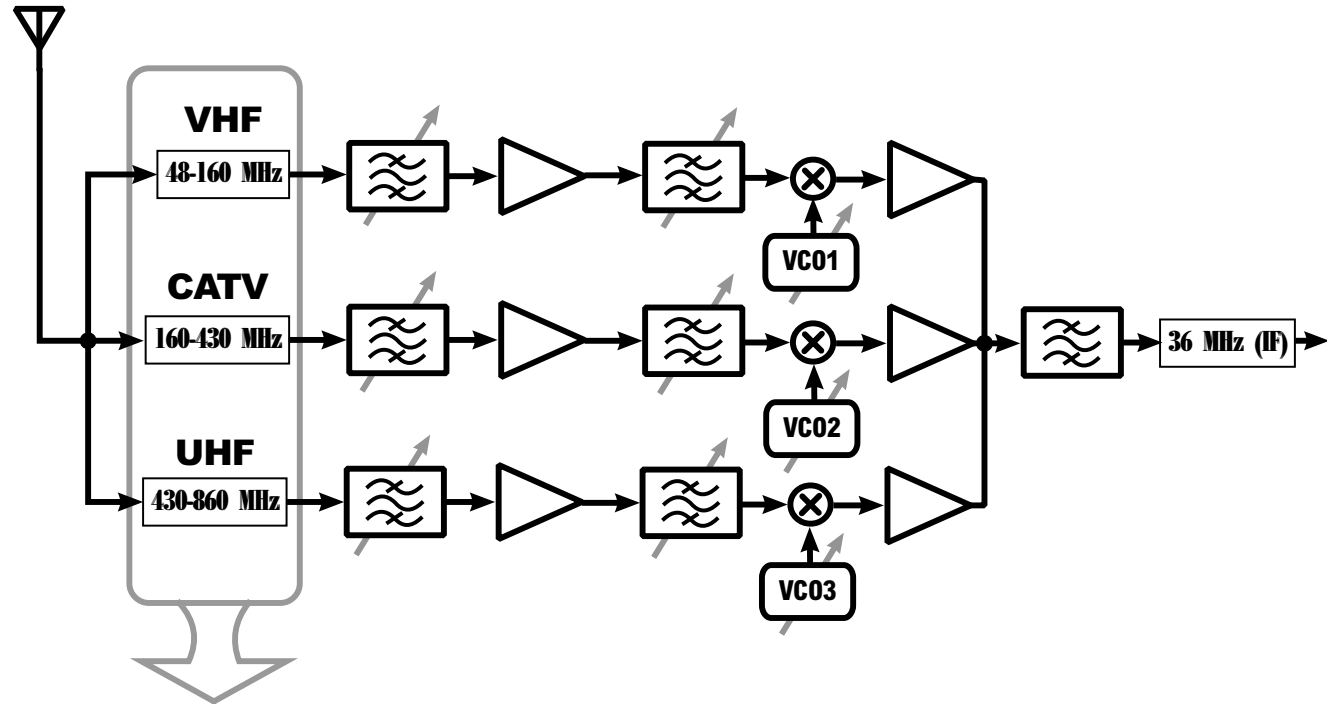



**Input Frequency Range
spans 4 octaves!**

- ✓ Mixers
- ✓ LNA and Variable Gain Amplifier
- ✓ Local Oscillator

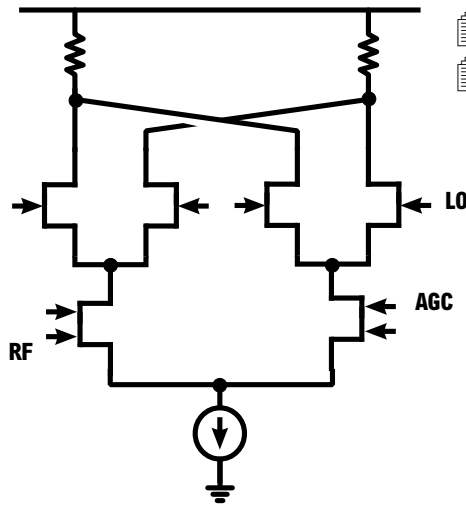Mixers and LO for Upconversion TV Tune





 Ablassmeier, *et al.*, Siemens, 1980


 Müller, *et al.*, Siemens, 1984

Off-chip oscillator




RF Range	40-900 MHz
IF	2500 MHz / 36 MHz
Conversion Gain	20 dB
Noise Figure	6-8 dB
In-channel signal causing 1% cross-modulation	20 mV

Low-Voltage TV Tuner

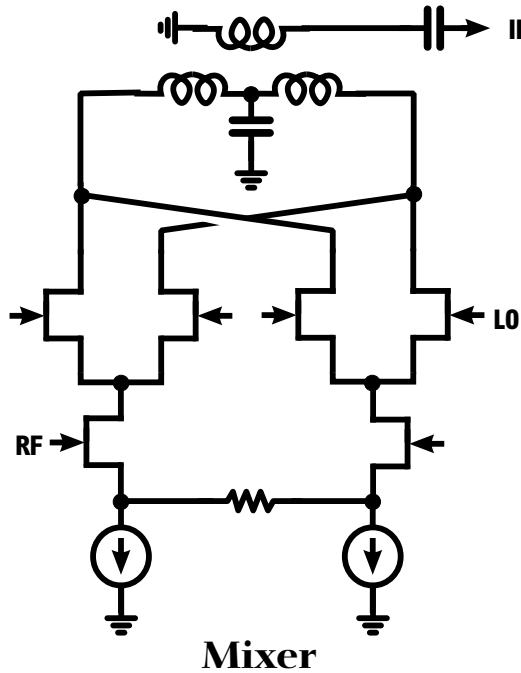 Mizukami, *et al.*, Hitachi, 1988
 Mizukami, *et al.*, Hitachi, 1992




RF Range	48-860 MHz
Conversion Gain	20-23 dB
Noise Figure	11-13 dB
3rd Order IM	-50 dB at -30 dBm inputs
Power Dissipation	225 mW from 5-V 135 mW from 3.3-V
Technology	1- μ m GaAs MESFET

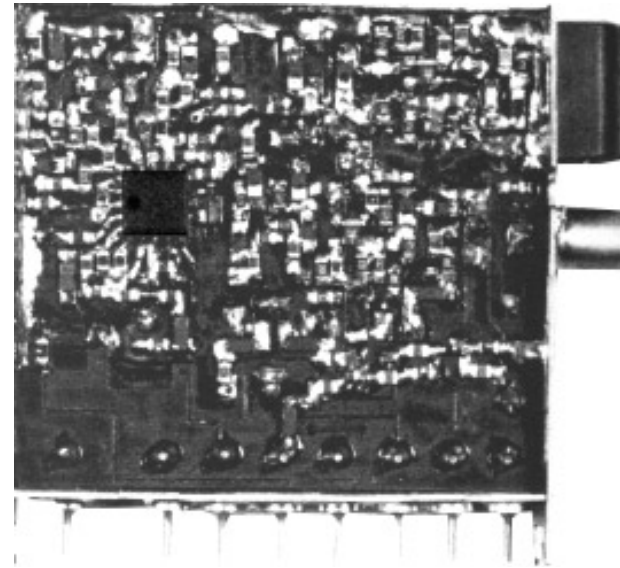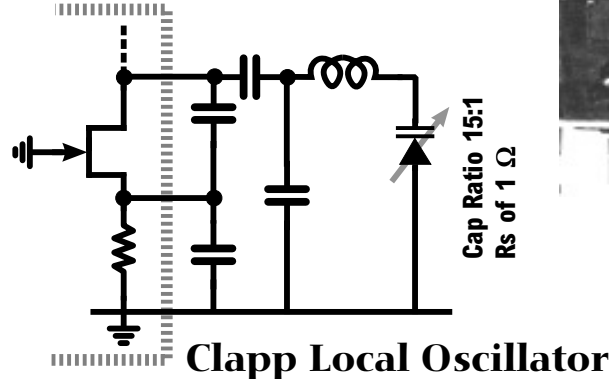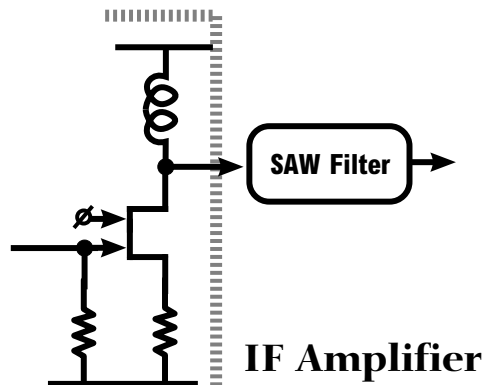


Tuner Assembly

Silicon TV Tuner ICs

📄 Fenk & Tauber, Siemens, 1986

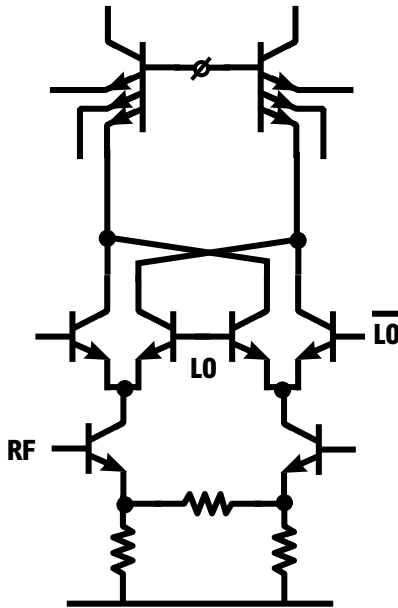

RF Amplifier & Mixer

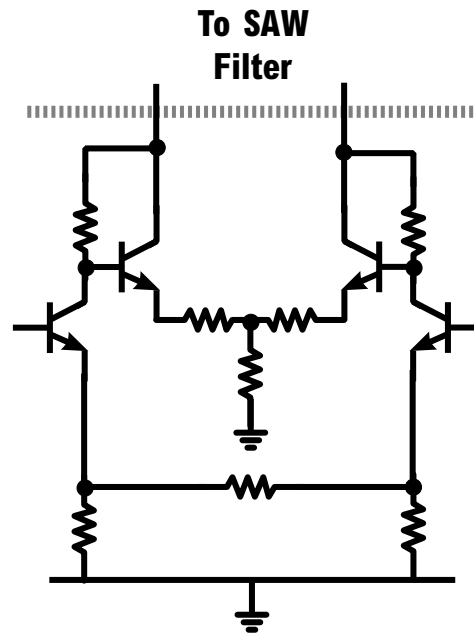

SAW Filter Driver


- Conventional single-conversion frequency plan
- Covers 54 MHz to 438 MHz (5 GHz bipolar process) in two separate sub-sections of IC



RF Range	175-462 MHz
IF	60 MHz
Conversion Gain	34 dB
Noise Figure	8.3-9 dB
In-channel signal causing 1% modulation	70 mV

📄 van Glabbeek, *et al.*, Philips, 1987


Includes UHF input (up to 900 MHz)

Highly Integrated TV Tuner

 Ducourant, *et al.*, LEP/Philips, 1989

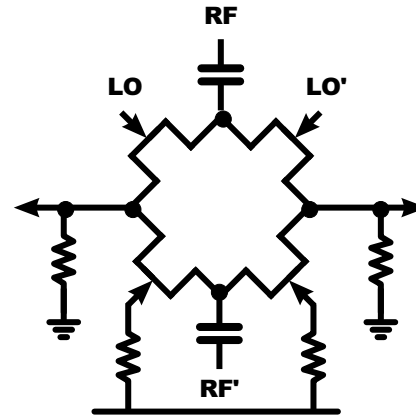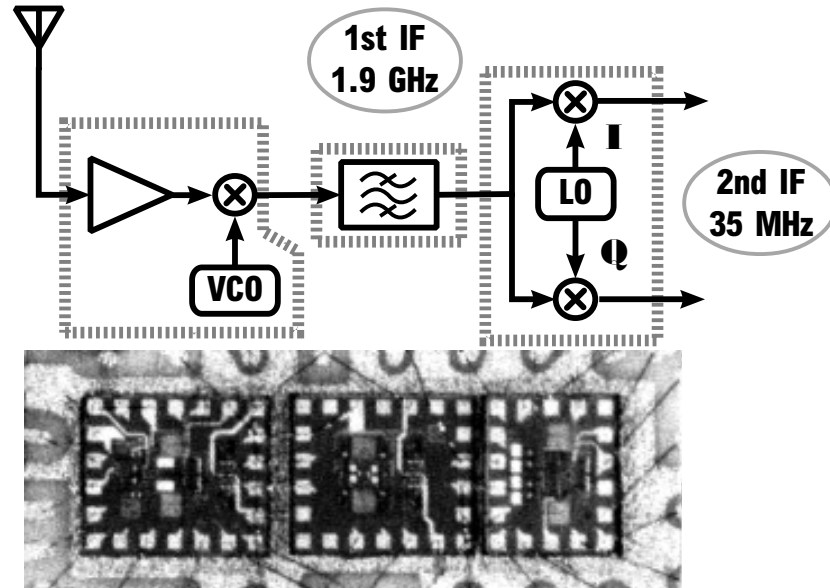

FET Switch Mixer

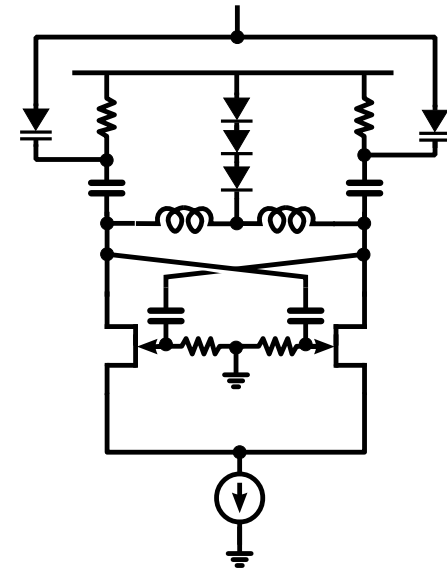

LC Tuned Multivibrator VCO

RF Range	48-860 MHz
Conversion Gain	18 dB
Noise Figure	12 dB
Input signal level for 1% cross-modulation	5.6 mV
Technology	0.7- μ m GaAs MESFET


- Eliminates *all* RF passive components!
- 1st IF filter is a GaAs tuned amplifier (4 dB down at $\Delta f=70$ MHz)
- On-chip *RC-CR* network to generate quadrature LO gives 60 dB image rejection, 70 dB after trim (channel independent)

RF ICs in Digital Cellular Telephones

☞ Fenk, *et al.*, Siemens, 1990

☞ Badura, Siemens, 1991

Receiver IC

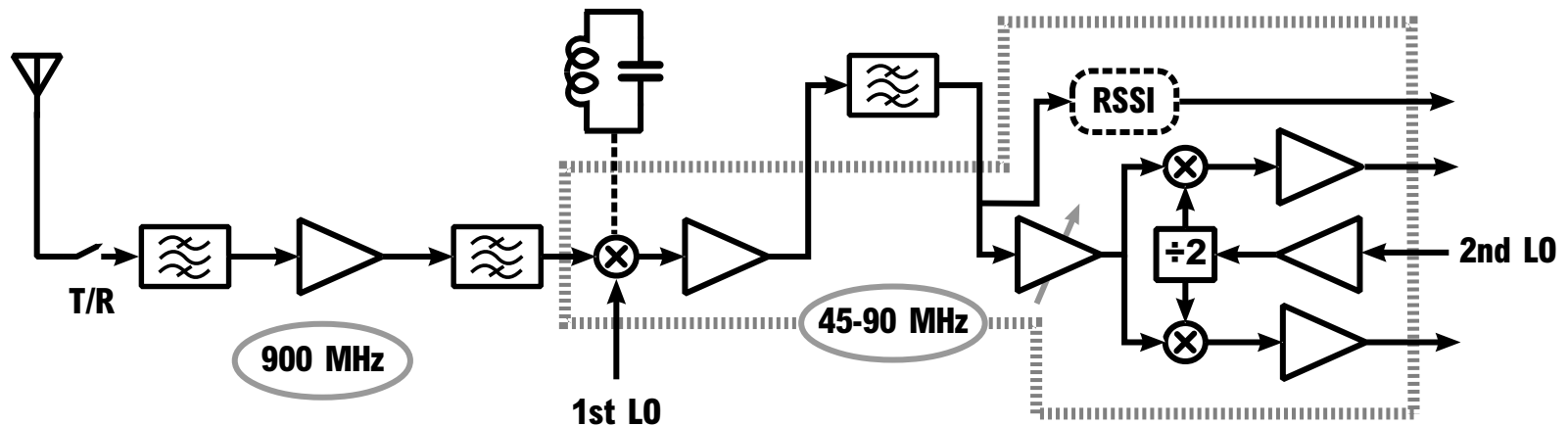


- Implemented in 7.5 GHz silicon bipolar technology
- Fully balanced signal path on IC
- 15 dB mixer conversion gain + 70 dB AGC range (implemented by cascade of four amplifiers with controlled degeneration resistance)
- 7 dB Noise Figure
- 27 mA drain from 4.5 to 5.5 V; 10 μ A in standby

RF ICs in Digital Cellular Telephones

☞ Fenk, *et al.*, Siemens, 1990


☞ Badura, Siemens, 1991

Transmitter IC

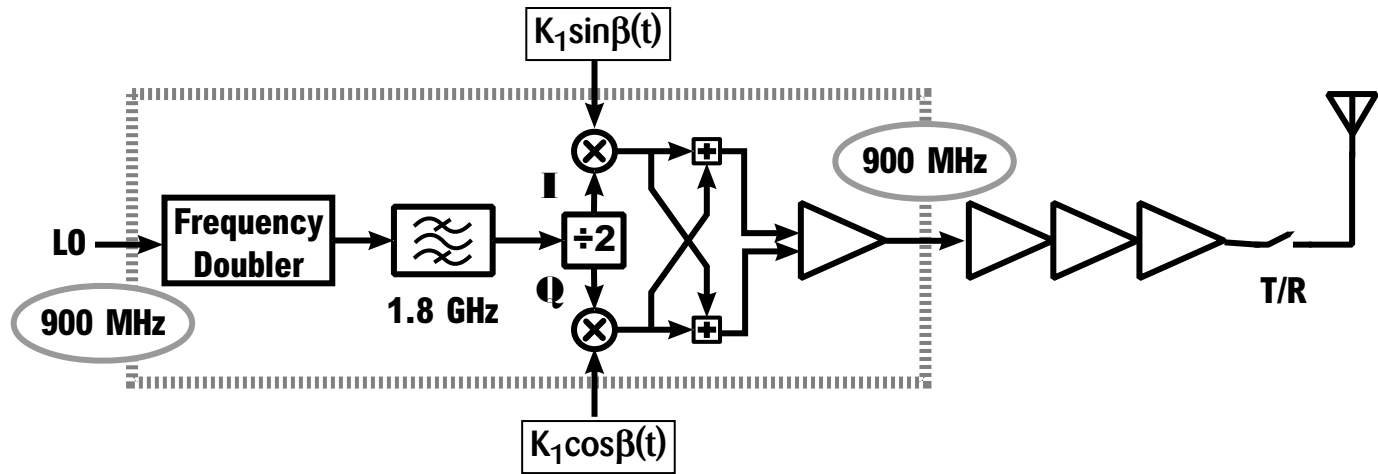

- One-step upconversion of complex baseband signal
GSM \Rightarrow phase-shift modulation (GSM)
- I-Q matching on-chip good enough ($< 2^\circ$ error) for:
Carrier suppression of 45 dB
SSB rejection of 45 dB
Intermod products less than 42 dB
- 40 mA drain from 4.5 to 5.8 V; 10 μ A standby
- 0 dBm drive into power amplifier
- Good isolation at 900 MHz on-chip; small leakage of intended sideband remodulates carrier to produce -57 dBc spur

RF ICs in Digital Cellular Telephones

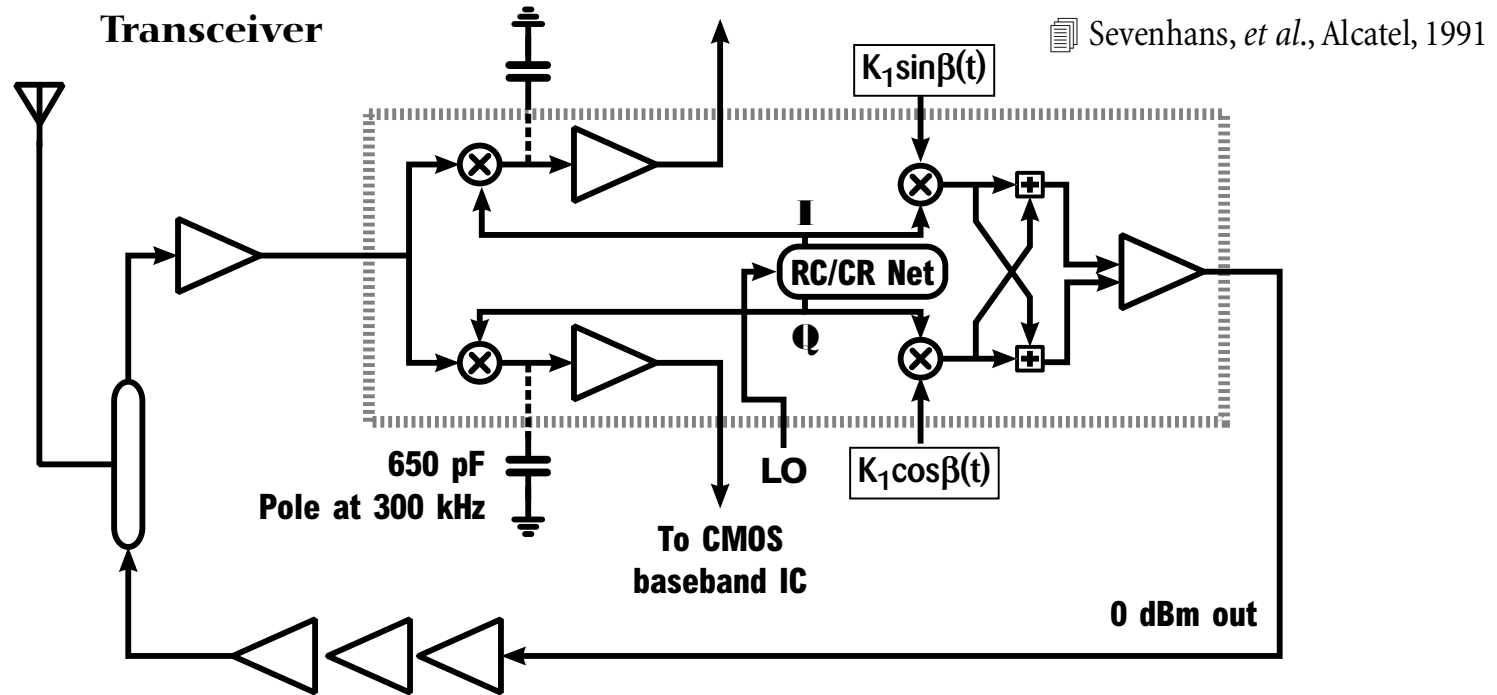


- Zero IF eliminates bandpass filters
- LNA has 17 dB gain, 3 dB NF
- Rcv mixer must withstand large (-6 dBm) blocking signals 6 MHz away from carrier
- Degenerated Gilbert cell used \Rightarrow 14 dB NF + 3 dB due to image noise in SSB rcvd signal

- Quadrature LO generated with RC/CR to reduce power dissipation; this needs adjustment to meet specs
- 9 GHz silicon bipolar IC (2.5 mm sq)
- Drains 25 mA in RX, 45 mA in TX from 5V supply
- Image suppression of 40 dB

RF IC for a Spread-Spectrum Radio


Devlin, *et al.*, GEC-Marconi, 1993

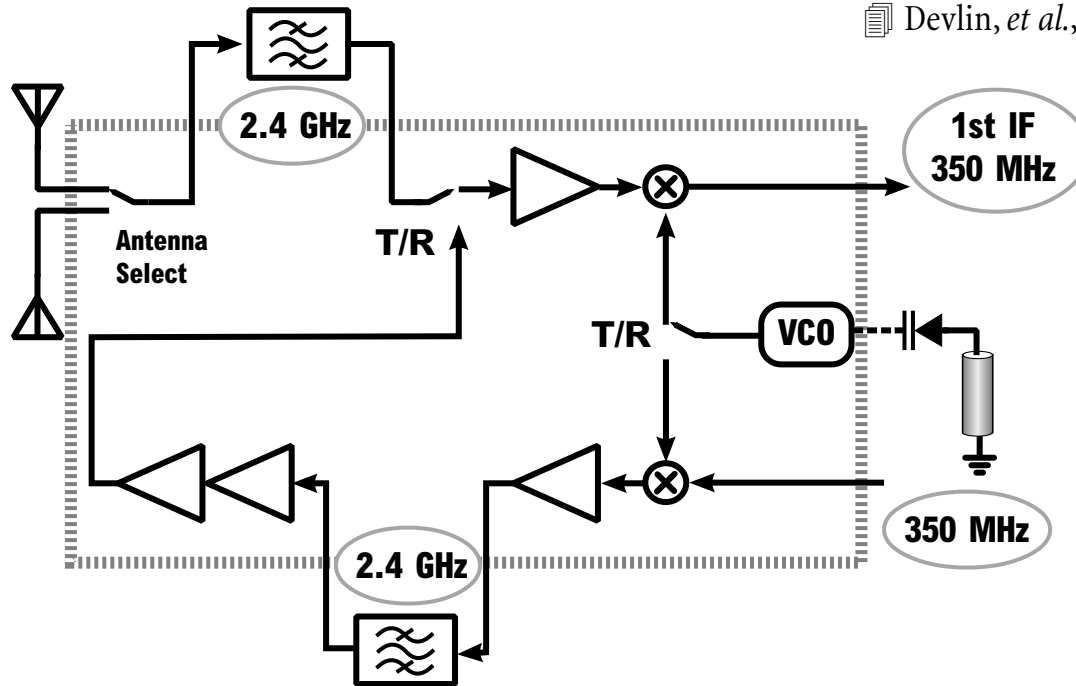

To silicon bipolar IC for IF
signal processing and
frequency de-spreading


- Monolithic GaAs transceiver IC for operation in the 2.4 - 2.48 GHz band
- For use in double-conversion architecture (thus 350 MHz first IF to reject image)
- Requires off-chip (dielectric resonator) passive bandpass filters
- On-chip switching for two-antenna diversity

Details of Spread-Spectrum IC

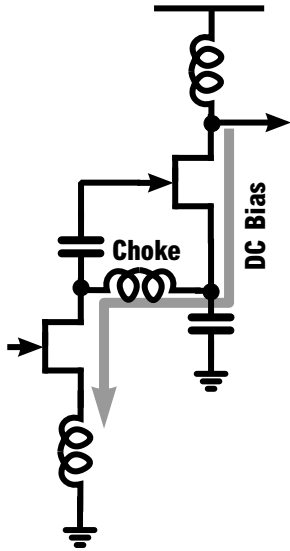


Low-Noise RF Amplifier

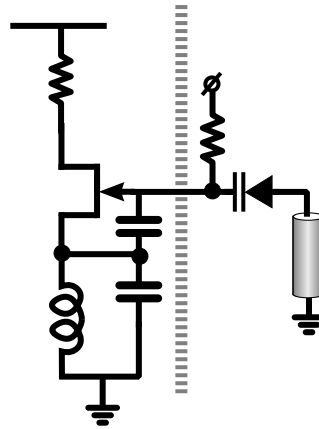- Noise matching with series feedback inductor
- Two cascaded gain stages share bias current



Voltage-Controlled Clapp Oscillator

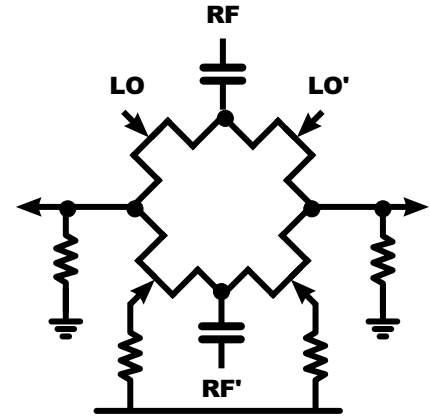
- Varactor affords tuning range of 150 MHz
- Phase noise is -122 dBc/Hz at a 1 MHz offset from carrier



Mixer in TX and RX

- High Linearity
- 6 dB conversion loss


Chip Performance

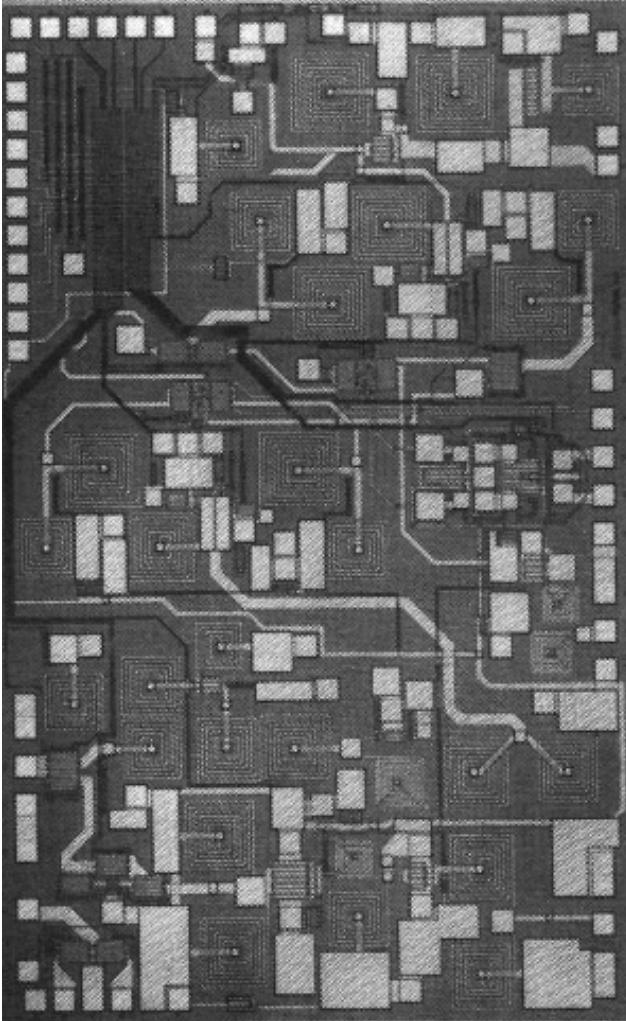


Transmit Level	Up to 21 dBm
Transmitter Gain	38 dB
Phase noise	-122 dBc/Hz at 1 MHz off carrier
Current Drain	220 mA from 5 V in transmit mode 30 mA in receive mode 0.5 mA in standby
Receiver Gain	14 dB
Net Noise Figure	4 dB (DSB)


More than 20 spiral inductors on-chip!


Power Amplifiers

 Takagi, *et al.*,
 Mitsubishi, 1992

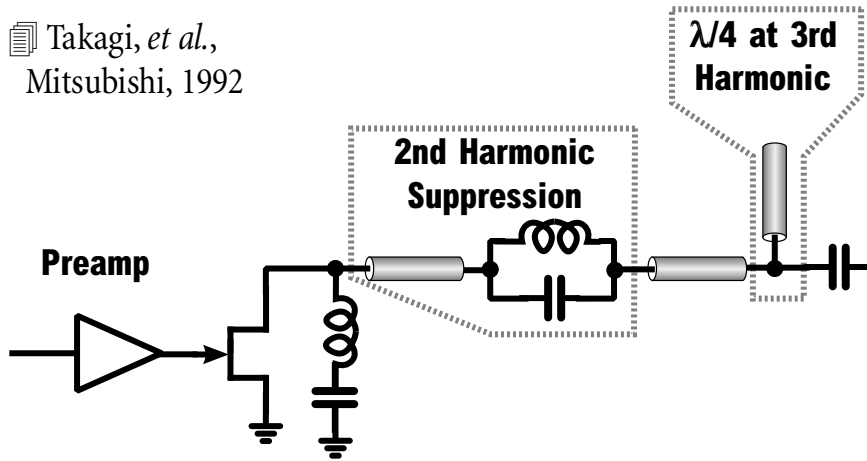

Peak Output Power	1.3 W from 5.5 V supply
Efficiency	0.63
2nd & 3rd Harmonics	-50 dBc and -40 dBc
Frequency Band	900 MHz

 Okabe, *et al.*,
 Hitachi, 1993

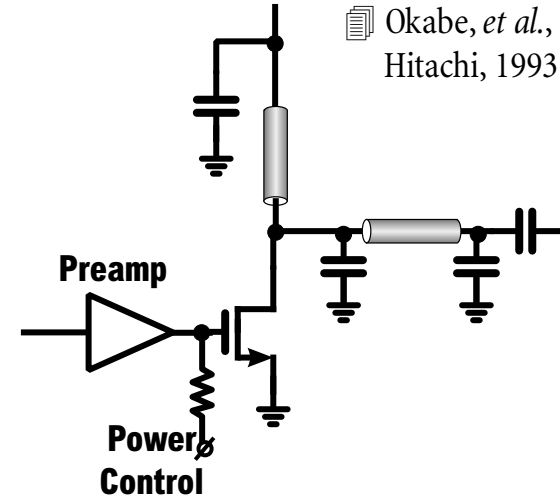


Peak Output Power	3.6 W from 6 V supply
Efficiency	35%
2nd & 3rd Harmonics	-45 dBc
Frequency Band	900 MHz

- Narrowband power amplifiers:
 Usually single transistors biased close to cutoff (for high power-conversion efficiency)
 Followed by filters to remove harmonics


- Efficiency at high frequencies determined by transistor f_T and parasitic capacitances

Signal Strength Indication Circuits


Logarithmic Amplifier

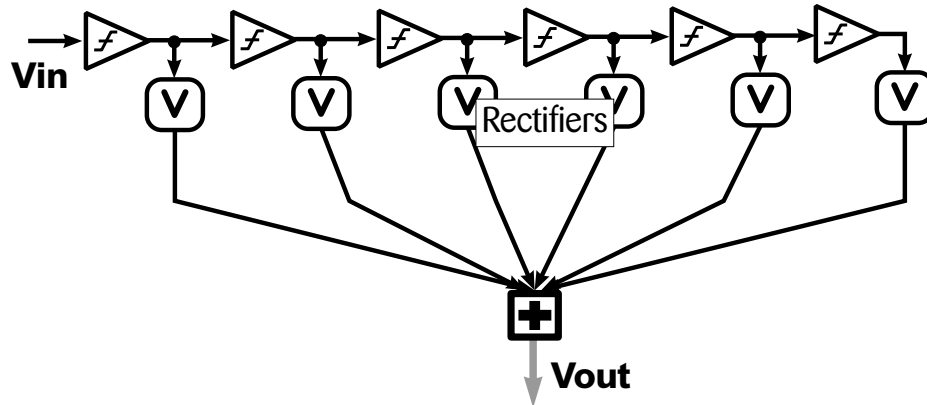

Input-Output Characteristic

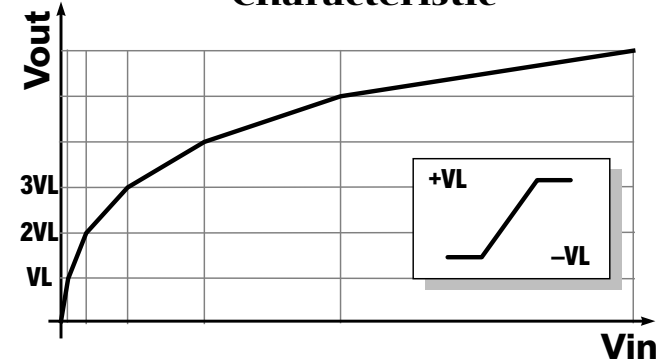


Single Stage in Logarithmic Amplifier

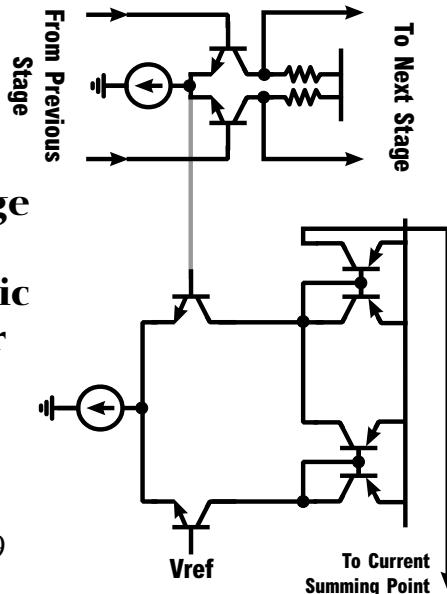






- Received signal-strength indication (RSSI) required for AGC and transmitted power control
- Logarithmic amplifiers with full IF bandwidth provide RSSI over 70 dB or more
- Approximate logarithm with cascade of AC coupled high-speed limiting amplifiers

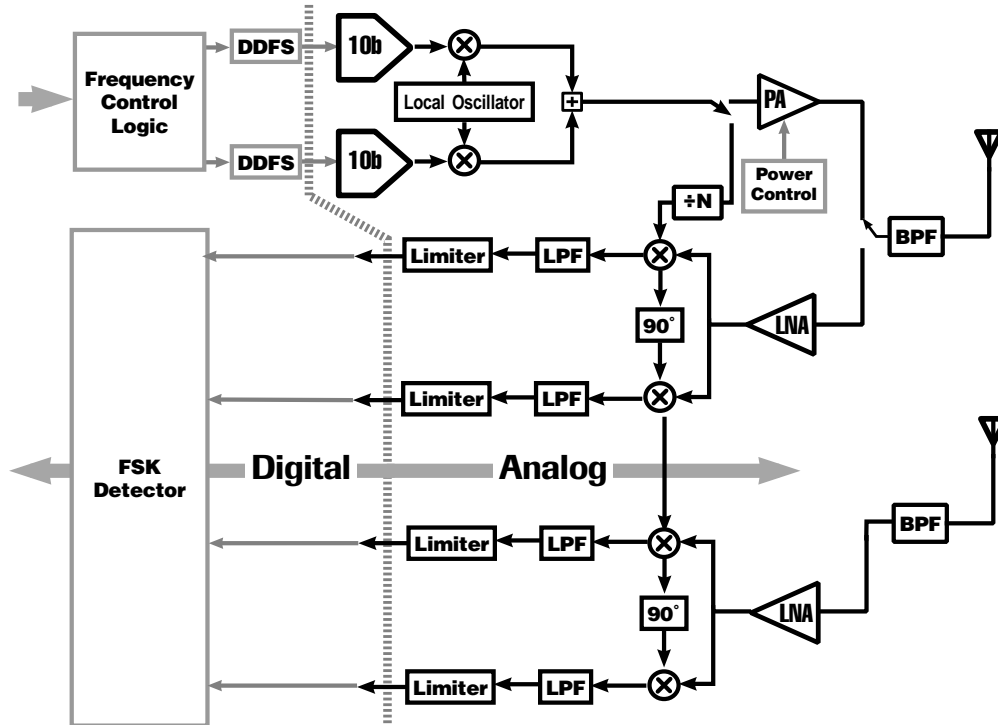The UCLA CMOS Frequency-Hopped Spread-Spectrum Transceiver






- Mixed analog-digital design, appropriate for CMOS
- Direct-conversion receiver eliminates off-chip filtering
- Binary FSK modulation may be detected with limiting, no AGC
- No high-speed equalization
- No high chip rate

On-Chip CMOS Tuned Amplifiers

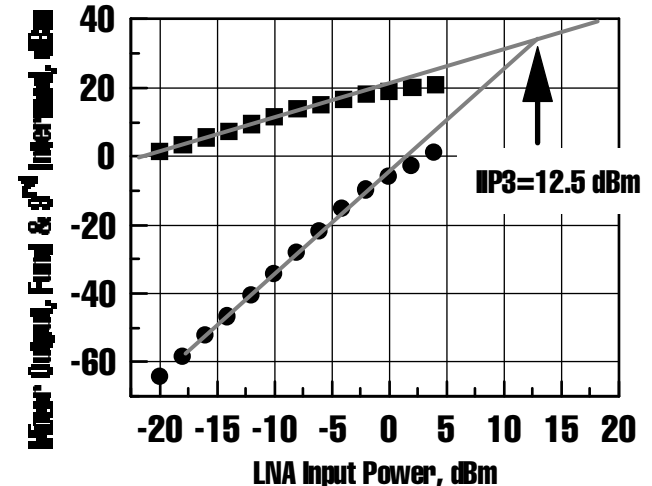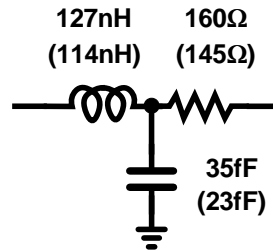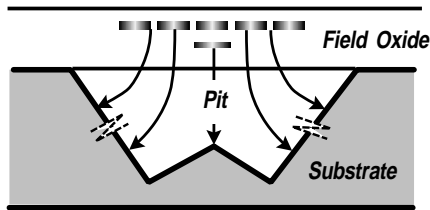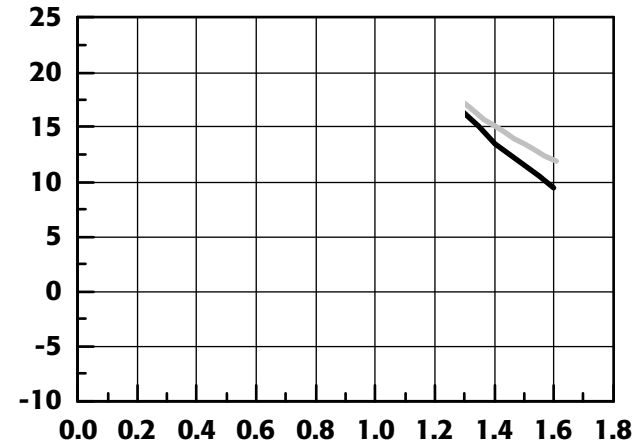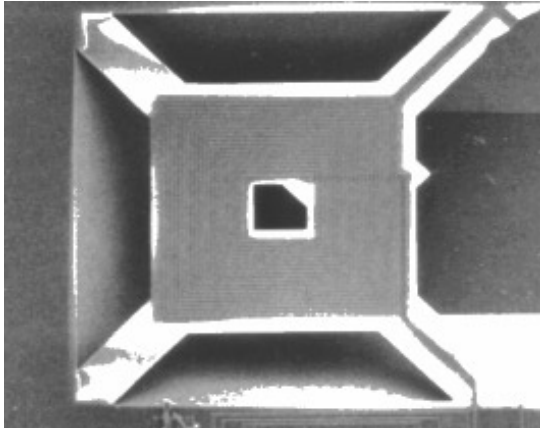



- 1 GHz front-end possible in 1- μm CMOS!
- High linearity, low noise (3 dB NF), low current drain ($\sim 8\text{mA}$) from 3-V
- Suspended inductor requires no extra masks

Frequency Synthesizer

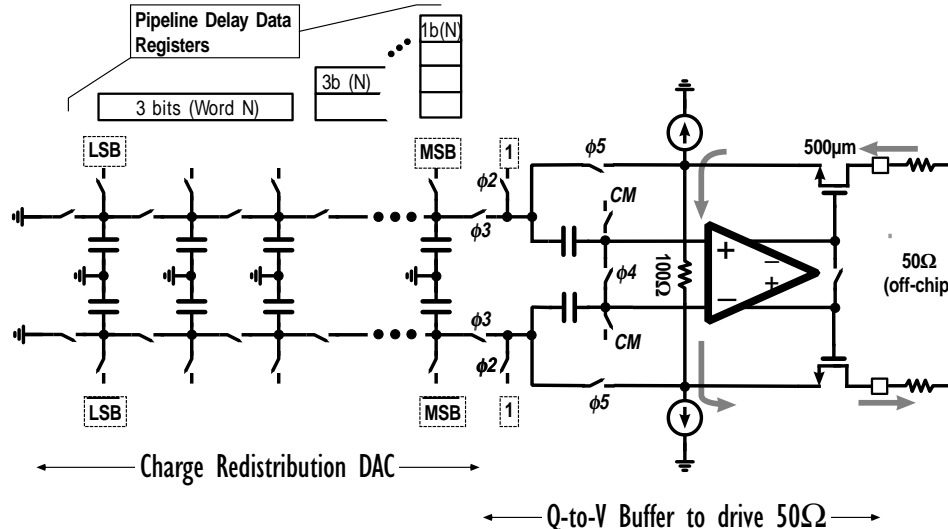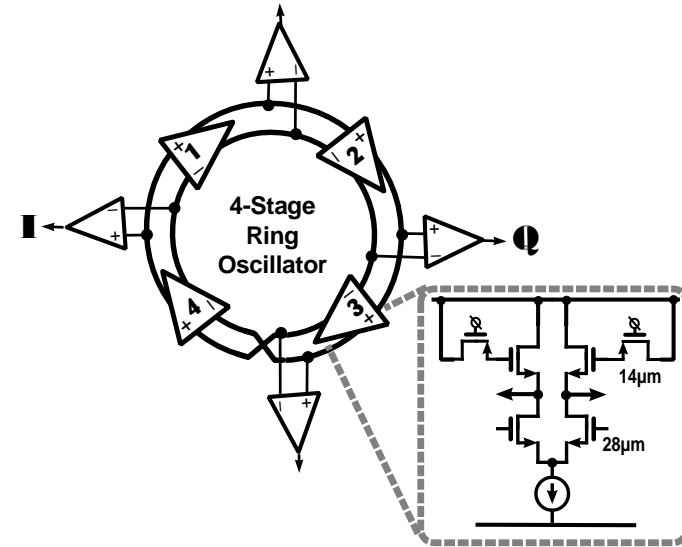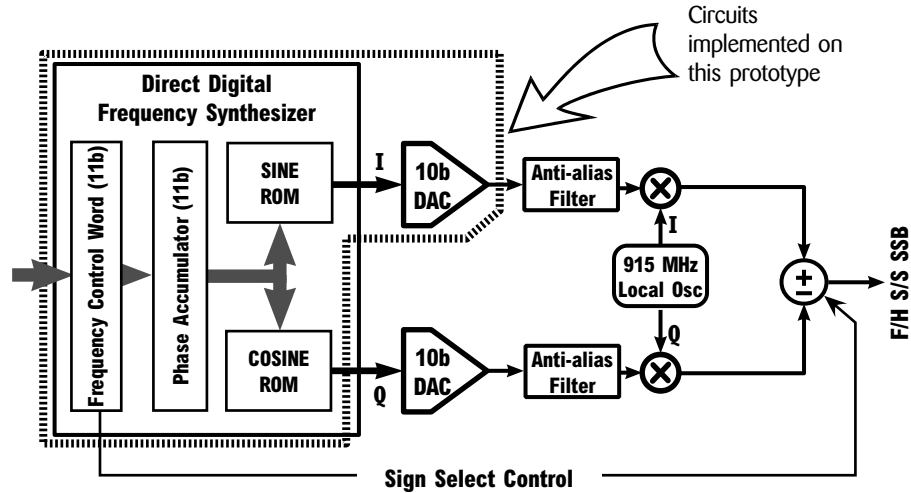

- DDFS-DAC shows worst-case -58 dBc spectral impurity, while dissipating 40 mW
- Fixed-frequency LO locked to 20 MHz crystal has -82 dBc/Hz phase noise at 100 kHz offset (10 mW)



Power Amplifier

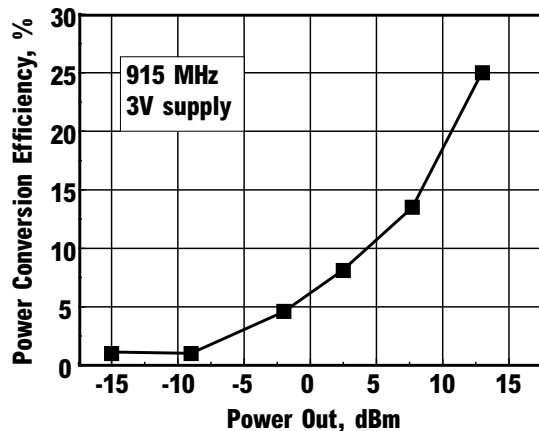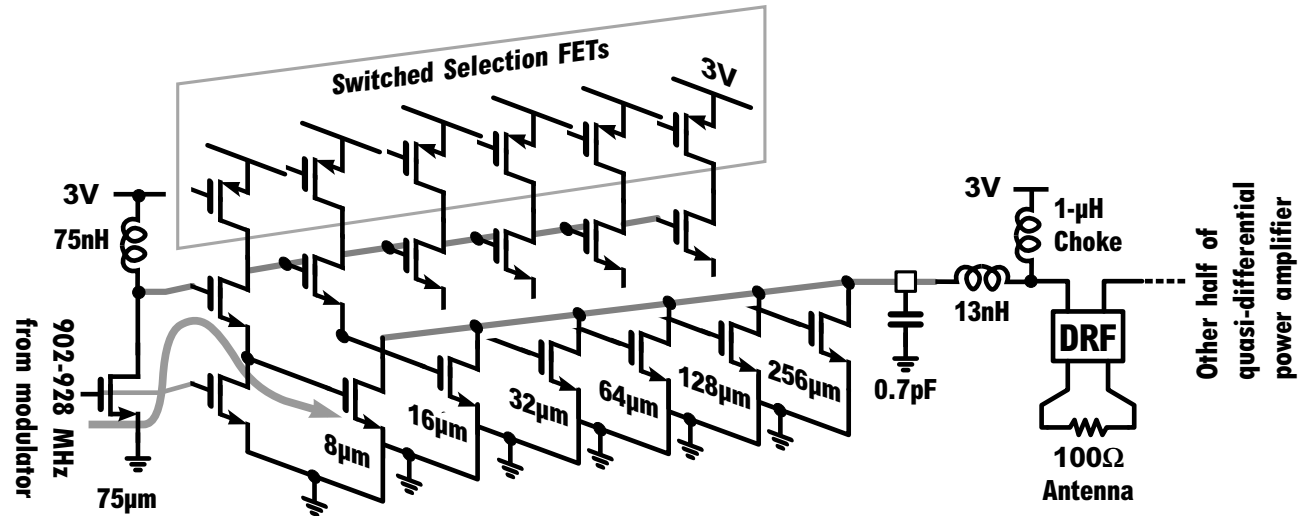

- Unique CMOS method to digitally select transmitted power level
- Good efficiency for low transmitted power levels
- Preamplifier with inductor load swings above power supply

Frequency Mixers

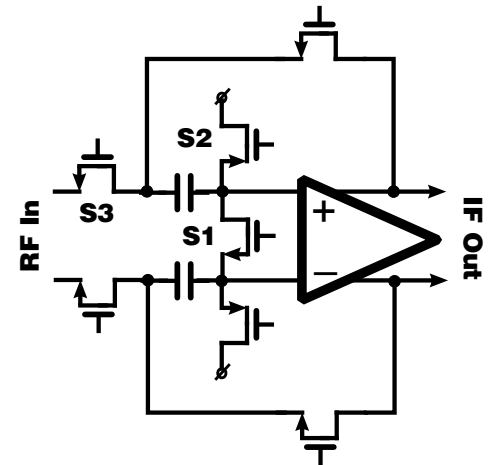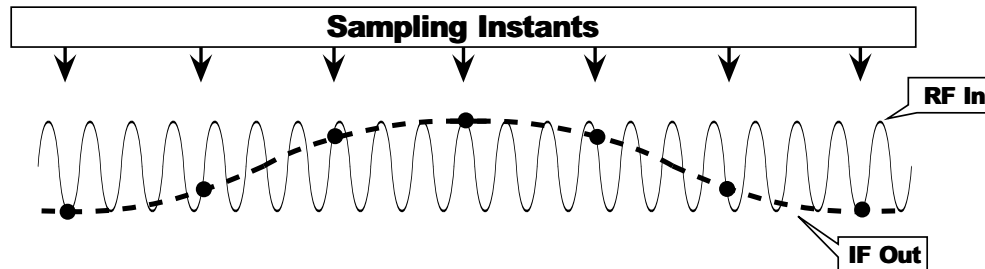- MOSFETs are much better suited to linear, continuous-time commutating mixers than BJTs!
- Alternative approach: Downconversion by direct sub-sampling of RF carrier (very high linearity, high NF)
- Subsampling mixer well-suited to direct-conversion receiver
- IIP3 of >20 dBm routinely possible, at typically 10 mW dissipation, in 1- μm CMOS



- Four-FET commutating switch well-suited to upconversion mixers