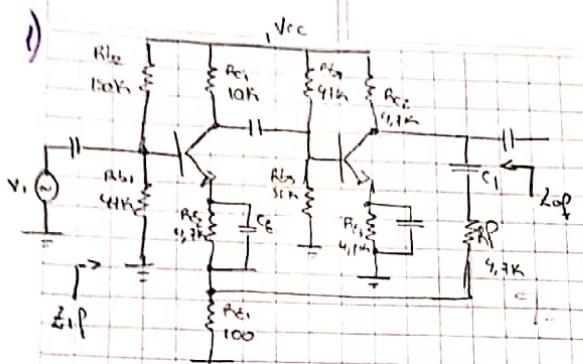


Realimentación negativa




$$R_{in} = 0$$

$$h_{fe} = 50$$

$$h_{ce} = 1.1k$$

Muestra transistores zeta

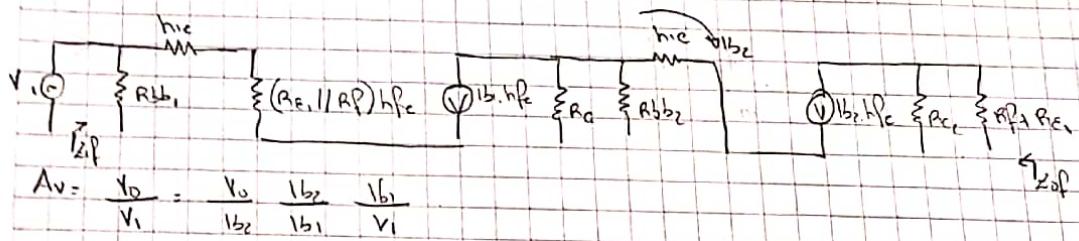

$$AV = \frac{V_o}{V_i} = \frac{V_o}{I_{b2}} \frac{I_{b2}}{I_{b1}} \frac{I_{b1}}{V_i}$$

$$-I_{b2}h_{fe} \cdot [R_{cc} \parallel (R_F + R_E)] = V_o \rightarrow V_o = -h_{fe} [R_{cc} \parallel (R_F + R_E)]$$

$$-I_{b1}h_{fe} \cdot \left[R_{cc} \parallel R_{bb2} \parallel h_{ce} \right] = I_{b2} \rightarrow \frac{I_{b2}}{I_{b1}} = -h_{fe} [R_{cc} \parallel R_{bb2} \parallel h_{ce}]$$

$$I_{b1} \cdot [h_{ce} + (R_E \parallel R_F) h_{fe}] = V_i \rightarrow \frac{I_{b1}}{V_i} = \frac{1}{h_{ce} + (R_E \parallel R_F) h_{fe}}$$

$$I_T = \frac{V_f}{R_{E1}} \quad I_f = \frac{V_f}{V_o f} \quad R_f = \frac{V_f}{V_o f} \Big|_{f=0} = \frac{R_{E1}}{R_{E1} + R_E}$$

$$V_o f = I_f (R_f + R_{E1}) \quad \frac{V_o f}{R_f R_{E1}} = \frac{V_f}{R_{E1}} \rightarrow \frac{V_f}{V_o f} = \frac{R_{E1}}{R_f + R_E}$$


$$AV_f = \frac{A_v}{1 + A_v B} = \frac{A_v}{1 + D}$$

$$Z_L = R_{bb1} \parallel \left[h_{ce} + (R_E \parallel R_F) h_{fe} \right]$$

Z.F.: ZL.D

$$Z_0 = R_{cc} \parallel (R_F + R_E)$$


$$Z_{op} = \frac{Z_0}{D}$$

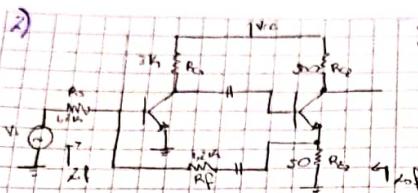

$V_f = 30V$

transistor com menor perda

?

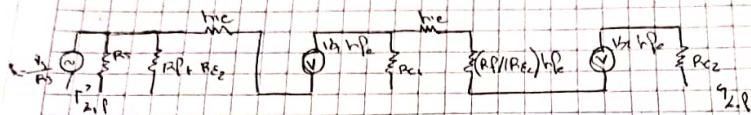

$$A_1 = \frac{V}{I_c} = \frac{V_{b2}}{I_{b2}} \frac{V_{b1}}{I_{b1}}$$

$$-I_{b2} h_{ie} = I_b \rightarrow \frac{I_b}{I_{b2}} = -h_{ie}$$

$$-I_{b2} h_{ie} \left\{ R_{ce} / \left[h_{ie} + (R_f / R_{fe}) h_{fe} \right] \right\} / \left[h_{ie} + (R_f / R_{fe}) h_{fe} \right] = I_{b2} \rightarrow \frac{I_{b2}}{I_{b1}} = \frac{-h_{ie} R_{ce} / \left[h_{ie} + (R_f / R_{fe}) h_{fe} \right]}{h_{ie} + (R_f / R_{fe}) h_{fe}}$$

$$I_c \left[R_{ce} / \left(R_f + R_{fe} \right) / h_{ie} \right] / h_{ie} = I_b \rightarrow \frac{I_{b1}}{I_c} = \frac{R_{ce} / \left(R_f + R_{fe} \right) / h_{ie}}{h_{ie}}$$

$$\frac{I_f}{R_f} = \frac{I_c}{h_{ie}} \quad R_f \frac{I_c}{I_f} = \frac{I_f}{I_{b1}} \quad \frac{I_f}{I_{b1}} = \frac{R_{ce} / \left(R_f + R_{fe} \right) / h_{ie}}{h_{ie}}$$

$$\frac{R_{ce} / \left(R_f + R_{fe} \right) / h_{ie}}{h_{ie} + (R_f / R_{fe}) h_{fe}} = \frac{I_f}{I_{b1}} \rightarrow \frac{I_f}{I_{b1}} = \frac{R_{ce} / \left(R_f + R_{fe} \right) / h_{ie}}{h_{ie} + (R_f / R_{fe}) h_{fe}}$$

$$A_f = \frac{A_1}{1 + \beta A_1} = \frac{A_1}{D}$$


$$Z_i = R_b / \left(R_f + R_{fe} \right) / h_{ie}$$

$$Z_o = \frac{Z_L}{D}$$

$$Z_o = R_{ce}$$

$$Z_o = Z_L D$$

NOTA

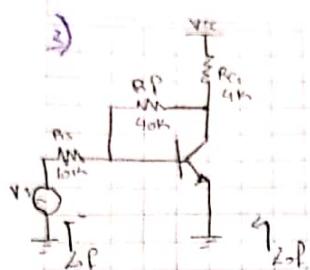


R_P
40k

h_{ie} , 1 , W_1

$h_{fe} > 0$

modular transistor model, good

$$I_b = \frac{V_b}{R_b}$$

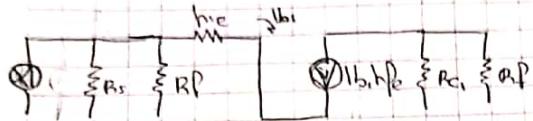

$$R_m = \frac{V_b}{I_b} = \frac{V_b}{I_b \cdot h_{ie}}$$

$$-I_b \cdot h_{fe} (R_C || R_P) V_b \rightarrow \frac{V_b}{I_b} = -h_{fe} (R_C || R_P)$$

$$I_s \cdot (R_b || R_P || h_{ie}) \frac{1}{h_{ie}} = I_b \rightarrow I_b = \frac{R_b || R_P || h_{ie}}{h_{ie}}$$

$$\frac{I_f}{V_f}$$

$$I_b P$$

$$V_f$$

$$\frac{I_f}{V_f} = \frac{I_b}{V_b} = \frac{I_f}{V_b} = \frac{1}{R_P}$$

$$r_{of} = I_f R_P \rightarrow \frac{I_f}{V_b} = \frac{1}{R_P}$$


$$R_m = \frac{R_m}{1 + \beta R_m} = \frac{R_m}{D}$$

$$Z_i = R_b || R_P || h_{ie}$$

$$Z_o = Z_o/D$$

$$Z_o = R_P || R_C$$

$$Z_o = Z_o/D$$

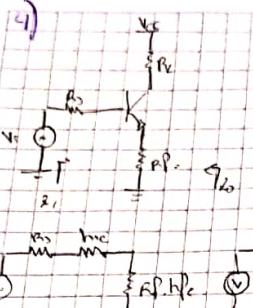

Dado:

$$G_m = -1 \text{ mA/V}$$

$$\beta = 50$$

$$h_{fe} = 100$$

$$R_s = 1k\Omega$$

$$R_L = 1k\Omega$$

Modo de trabajo estable:

$$\begin{cases} I_C = I_B \\ V_E = V_B \end{cases}$$

Dado:

operación

en lazo

$$G_m = G_m D = -50 \text{ mA/V}$$

$$\begin{aligned} &V_o = \frac{V_s}{R_s + R_p} = \frac{V_s}{1k\Omega + R_p} = \frac{V_s}{1k\Omega + h_{fe} R_p} = \frac{V_s}{1k\Omega + 100 R_p} = \frac{V_s}{1k\Omega + 100 \cdot 1k\Omega} = \frac{V_s}{101k\Omega} = \frac{V_s}{101} \quad | \quad V_s = 25V \rightarrow V_o = \frac{25}{101} \approx 0.25V \\ &\beta = h_{fe} : \text{Gráf. } G_m = \frac{G_m}{D} = \frac{G_m}{1 + G_m \beta} \rightarrow 1 + G_m \beta = \frac{G_m}{G_m \beta} \rightarrow \beta = \frac{G_m + 1}{G_m} = \frac{1}{G_m} + 1 = \frac{1}{G_m} \quad | \quad G_m = \frac{1}{h_{fe}} = \frac{1}{100} = 10^{-2} \text{ S} \\ &\beta = \frac{1}{G_m} - 1 = -990 \quad | \quad R_p = 980 \approx 1k\Omega \\ &G_m = \frac{I_C}{V_S} = \frac{I_C}{100} = \frac{10}{100} = 0.1 \text{ A/V} \\ &-h_{fe} R_p = I_C \rightarrow \frac{I_C}{100} = -h_{fe} R_p = -100 \cdot 100 = -10000 \text{ A} \end{aligned}$$

$$\begin{aligned} &(R_s + h_{ie} + R_p h_{fe}) I_{B1} = V_S \rightarrow I_{B1} = \frac{V_S}{R_s + h_{ie} + R_p h_{fe}} \\ &: G_m = -h_{fe} \cdot \frac{1}{R_s + h_{ie} + R_p h_{fe}} \rightarrow R_s + h_{ie} + R_p h_{fe} = -\frac{h_{fe}}{G_m} \rightarrow h_{ie} = \frac{-h_{fe} - R_s - R_p h_{fe}}{G_m} \end{aligned}$$

$$\text{Póngase en el pl. cc para } h_{fe}!! \quad G_m = -h_{fe} \frac{1}{R_s + h_{ie} + R_p h_{fe}} \quad | \quad h_{ie} = |V_b|$$

$$\text{AvP: } G_m P_r R_L \rightarrow R_L = \frac{A_v P_r}{G_m} = \frac{4k}{0.1} = 40k \rightarrow |P_r = 4k|$$

$$Z_1 = R_s + h_{ie} + R_p = 3k$$

$$|Z_1| = Z_1 \cdot D = 150k$$

$$|h_{ie}| = \frac{|h_{fe}| \cdot 25V}{100} \rightarrow |I_{C0}| = \frac{|h_{fe}| \cdot 25V}{h_{ie}} = 39mA$$

NOTA

Análisis

5-A)

Resistores: $R_1 = 10k\Omega$, $R_2 = 10k\Omega$, $R_3 = 10k\Omega$, $R_4 = 10k\Omega$, $R_5 = 2k\Omega$, $R_6 = 1k\Omega$, $R_L = 50\Omega$, $V_{CC} = 10V$, $V_{BE} = 0.7V$, $I_{CQ} = 1mA$.

Currents: $I_S = \frac{V_{CC}}{R_1 + R_2} = 1mA$, $I_B = \frac{I_S}{h_{FE}} = 0.1mA$, $I_C = I_S - I_B = 0.9mA$.

Output voltage: $V_{OF} = V_{CC} - I_C(R_4 + R_5) = 8.2V$.

Output resistance: $Z_{OF} = h_{OC} = R_L = 50\Omega$.

Input resistance: $Z_{IF} = h_{IE} = \frac{V_{IF}}{I_B} = 10M\Omega$.


Input current: $I_{IF} = \frac{V_{IF}}{R_1 + R_2} = 1mA$.

Output power: $P_{OF} = I_C V_{OF} = 0.9mA \cdot 8.2V = 7.38mW$.

Input power: $P_{IF} = I_{IF} V_{IF} = 1mA \cdot 10V = 10mW$.

NOTA

5 b)

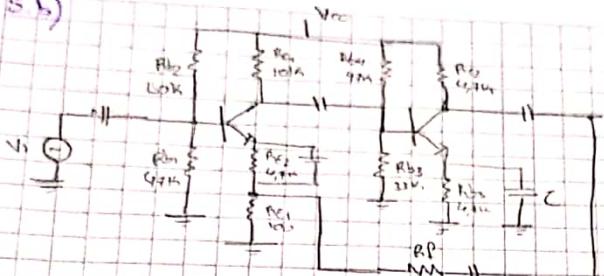

Magnetooptik + magnetische

$$A_vP = 45,4$$

$$\Delta A_vP = 0,2117$$

$$\Delta A_v = 5\%$$

$$A_vP = \frac{A_v}{D} \quad \therefore \quad \Delta A_vP = \frac{\Delta A_v}{D} \rightarrow D = \frac{\Delta A_v}{\Delta A_vP} = 18,4 \quad \therefore A_v = A_vP \cdot D = 837,63$$

$$V_f = \frac{R_f}{R_{E1} + R_f} V_o$$

$$|B = \frac{V_2}{V_L} = \frac{V_f}{V_{oP}}| \cdot 18,0$$

$$V_{oP} = (R_f + R_{E1}) I_{oP}$$

$$V_{oP} = R_{E1} I_{oP}$$


$$\frac{V_{oP}}{R_f + R_{E1}} = \frac{V_f}{R_{E1}} \rightarrow \frac{V_f}{V_{oP}} = \frac{R_{E1}}{R_f + R_{E1}}$$

$$A_vP = \frac{A_v}{1 + A_v \beta} \rightarrow 1 + A_v \beta = \frac{A_v}{A_vP} \rightarrow \beta = \left(\frac{A_v}{A_vP} - 1 \right) \frac{1}{A_v} = \frac{1}{A_vP} - \frac{1}{A_v}$$

$$\beta = \frac{R_{E1}}{R_f + R_{E1}} \quad \therefore \quad \left(\frac{1}{A_vP} - 1 \right) = \frac{R_{E1}}{R_f + R_{E1}} \rightarrow R_f + R_{E1} = \frac{R_{E1}}{\left(\frac{1}{A_vP} - 1 \right)} \rightarrow R_f = \frac{R_{E1}}{\left(\frac{1}{A_vP} - 1 \right)} - R_{E1} = 4700$$

$$\therefore | R_f: 4700 \Omega |$$

S.C)

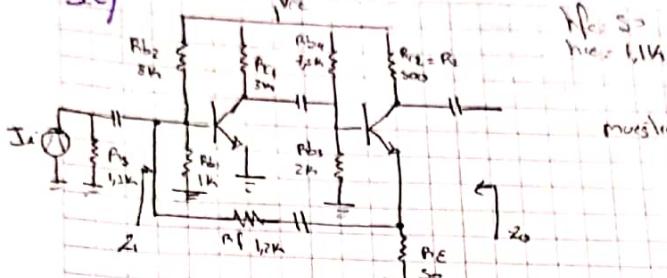 $h_{FE} \approx 50$
 $h_{ie} \approx 1,1K$

muitas correntes - rede paralelo.

$$\left(\frac{I_S}{R_E + R_{bb1}} \right) \parallel \left(\frac{I_{bb1} h_{fe}}{R_{bb1}} \right) \parallel \left(\frac{I_{bb2} h_{fe}}{R_{bb2}} \right) \parallel \left(\frac{(R_f / R_E) h_{fe}}{R_L} \right)$$

$$A_v = \frac{I_C}{I_S} = \frac{1}{R_E} \frac{1}{R_{bb1}} \frac{1}{R_{bb2}}$$

$$-I_{bb2} h_{fe} = I_C \rightarrow \frac{1}{R_E} = -h_{fe}$$

$$2k \parallel 1578 \parallel (1,1K + (18)50) = 798$$

$$-I_{bb2} h_{fe} \cdot \left\{ R_E \parallel R_{bb2} \parallel \left[h_{ie} + (R_f / R_E) h_{fe} \right] \right\} \frac{1}{h_{ie} + (R_f / R_E) h_{fe}} = \frac{I_{bb2}}{I_{bb1}} \quad : \frac{I_{bb2}}{I_{bb1}} = -1,40$$

$$I_S \cdot \left[R_E \parallel (R_f / R_E) \parallel R_{bb2} \parallel h_{ie} \right] \frac{1}{h_{ie}} = I_{bb1}$$

$$\frac{R_f}{R_E} = \frac{R_f}{R_E + R_{bb1}} \quad \frac{R_f}{R_E} = \frac{R_f}{R_E + R_{bb2}}$$

$$B = \frac{I_C}{I_S} = \frac{R_f}{R_E + R_{bb1}}$$

$$V_{of} = R_E \parallel R_f \quad I_{of}$$

$$V_{if} = R_f \parallel R_E \quad I_{if}$$

$$\frac{I_{of}}{I_{if}} = \frac{R_f \parallel R_E}{R_E + R_f} = \frac{R_E}{R_E + R_f}$$

$$A_{IP} = \frac{A_1}{1 + B A_1} = \frac{A_1}{B}$$


$$Z_1 = (R_f + R_E) \parallel R_{bb1} \parallel h_{ie}$$

$$Z_{1f} = Z_1 / D$$

$$Z_0 = R_L$$

$$Z_{of} = Z_0 / D$$

5D)

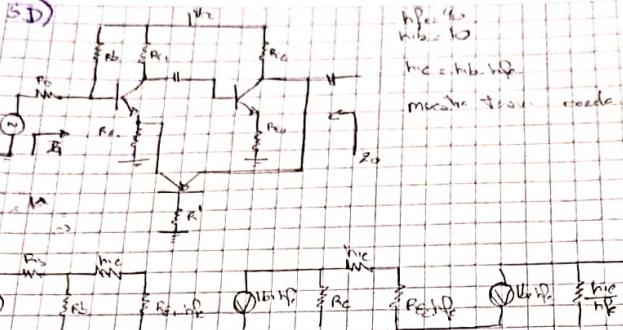

$$hfe \gg 100$$

$$hfe = hfe \cdot hfe$$


misurare \rightarrow β \rightarrow $\beta = hfe$

$$\Delta v = \frac{V_L}{V_S} = \frac{V_C}{V_S} \frac{h_{fe}}{h_{fe} + h_E} \frac{V_L}{R_L}$$

$$+ h_{fe} \cdot h_E \left[\left(\frac{h_{fe} + h_E}{h_{fe}} \right) \frac{V_L}{R_L} \right] \rightarrow \frac{V_L}{V_S} = -h_E \cdot \left[\left(\frac{h_{fe} + h_E}{h_{fe}} \right) \frac{V_L}{R_L} \right]$$

$$- h_E \cdot h_E \cdot R_C \parallel \left(h_{fe} + h_E \cdot h_E \right) \frac{1}{h_{fe} \cdot h_E} = h_{fe} \rightarrow \frac{1}{h_{fe}} = \frac{h_E}{h_{fe} \cdot h_E} \parallel \left(h_{fe} + h_E \cdot h_E \right)$$
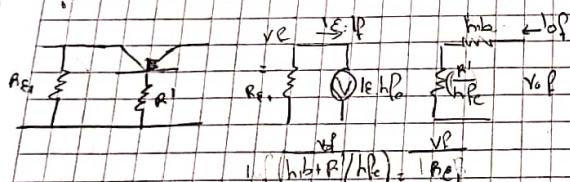
$$\frac{V_L}{V_S} = \frac{h_E}{h_{fe} + h_E \cdot h_E}$$



$$\beta = \frac{V_S}{V_L} = \frac{V_E}{V_L}$$

$$V_E = I_E \cdot h_E \quad V_L = I_C \cdot R_C$$

$$\frac{V_E}{V_L} = \frac{I_E \cdot h_E}{I_C \cdot R_C} = \frac{h_E}{h_E + R_C/h_E}$$

$$\Delta v_f = \frac{\Delta v}{1 + \Delta v}$$


$$Z_L = \left[R_C \parallel h_E + R_C/h_E \right] \rightarrow m \gg m \rightarrow m \gg R_C$$

$$Z_0 = R_C \parallel \left(h_E + \frac{R_C}{h_E} \right)$$

$$Z_0^f = Z_0 \cdot D$$

$$Z_0 f = Z_0 / D$$

NOTA

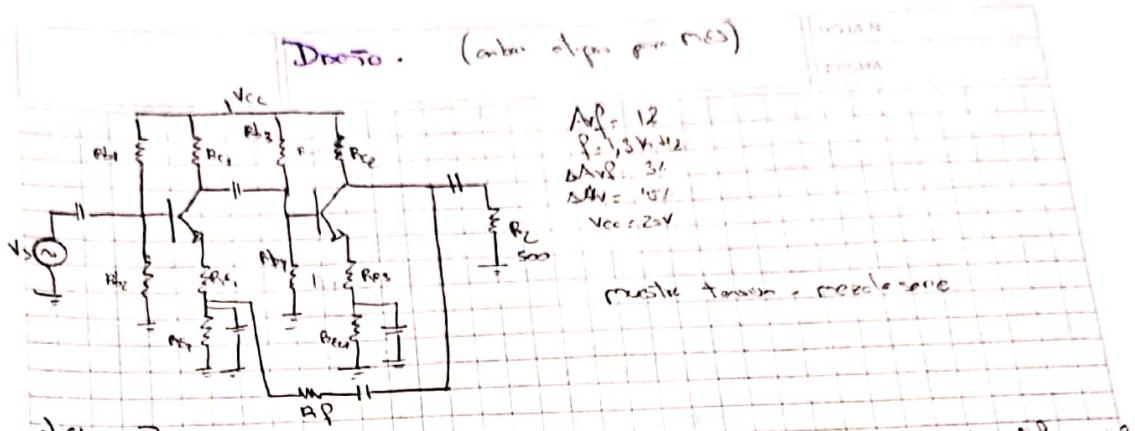

$$A_{Vp} = 12$$

$$\beta = 3 \times 10^3$$

$$bA_{Vp} = 36$$

$$\Delta V = 15V$$

$$V_{cc} = 25V$$

muito tempo e trabalho

1) Calculo B

$$B = \frac{\Delta A_{Vp}}{\Delta A_{Vf}} \quad D = \frac{1}{S} = \frac{\Delta V}{\Delta A_{Vp}} = \frac{q_3 - 15}{3} \rightarrow [D = 5] \quad \therefore N_f = \frac{A_{Vp}}{D} \rightarrow N_f = \frac{A_{Vp}}{5} = 180 \quad \boxed{180}$$

$$A_{Vp} = \frac{A_V}{1 + A_{Vp}} \rightarrow A_V = A_{Vp} \cdot \frac{1}{1 + A_{Vp}} \rightarrow \beta = \frac{A_V}{A_{Vp} \cdot A_f} = \frac{1}{1 + A_{Vp}} = 0,077 \quad \boxed{\beta = 0,077}$$

2) Análise de EC para largura de saída amplificadora

Definimos: $I_{CQ} = S_{NP}$ $V_{CE} = \frac{V_{cc}}{10} = I_{CQ} (R_{C3} + R_{E4}) \rightarrow R_{C3} + R_{E4} = \frac{V_{cc}}{10 \cdot I_{CQ}}$

$$V_{ceo} = 10V$$

$$V_{cc} = 22V$$

$$V_{cc} - I_{CQ} R_{C2} - V_{ceo} - I_{CQ} (R_{E3} + R_{E4}) = 0$$

$$R_{C2} = \frac{V_{cc} - V_{ceo} - I_{CQ} (R_{E3} + R_{E4})}{I_{CQ} \cdot 2}$$

$$R_{bb2} = \frac{\beta (R_{E3} + R_{E4})}{10}$$

$$= 10$$

$$V_{bb} = I_{CQ} (R_{bb2}) - V_{be} - I_{CQ} (R_{E3} + R_{E4}) \rightarrow R_{bb2} = \frac{R_{bb2}}{1 - \frac{V_{bb}}{V_{cc}}} = \frac{R_{bb2}}{\frac{V_{bb}}{V_{cc}}} = \frac{R_{bb2}}{V_{bb}/V_{cc}}$$

P/MES

$$I_{CQ,mes} = \frac{V_{cc}}{R_{cc} + R_{CA}} = \frac{V_{cc}}{(R_{C2} + R_{E3}) + (\beta C_2 / R_i)}$$

$$V_{bb2,mes} = I_{CQ,mes} (R_{bb2} - (R_{E3} + R_{E4})) - V_{be} \quad \therefore R_{bb2,mes} = \frac{R_{bb2}}{1 - \frac{V_{bb2,mes}}{V_{cc}}}$$


$$h_{FE}: 25mV/hFE$$

$$I_{CQ2,mes}$$

$$R_{bb2} = \frac{R_{bb2}}{\frac{V_{bb2,mes}}{V_{cc}}} =$$

$$\frac{V_{bb2,mes}}{V_{cc}}$$

Gráfica

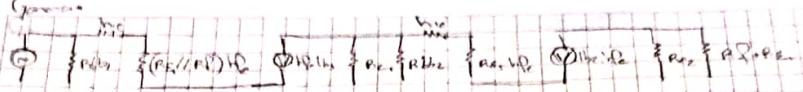


$$\text{Av: } \frac{V_o}{V_s} = \frac{V_o}{R_s + \frac{1}{C_1 s + R_1}}$$


$$-1\text{Hz} \cdot 1\text{Hz} \cdot R_s \parallel (R_1, C_1) = V_o \rightarrow \frac{V_o}{V_s} = -1\text{Hz} \cdot [R_s \parallel (R_1, C_1)]$$

$$-1\text{Hz} \cdot 1\text{Hz} \cdot \left[R_s \parallel \frac{1}{R_1 + \frac{1}{C_1 s}} \right] = \frac{1}{R_s + \frac{1}{C_1 s + R_1}} = 1\text{Hz}$$

$$\frac{V_o}{V_s} = \frac{-1\text{Hz}}{R_s + \frac{1}{(R_1, C_1) s + R_1}} = \frac{1\text{Hz}}{\frac{1}{R_s + \frac{1}{(R_1, C_1) s + R_1}}} = \frac{1}{R_s + \frac{1}{(R_1, C_1) s + R_1}}$$

NOTA

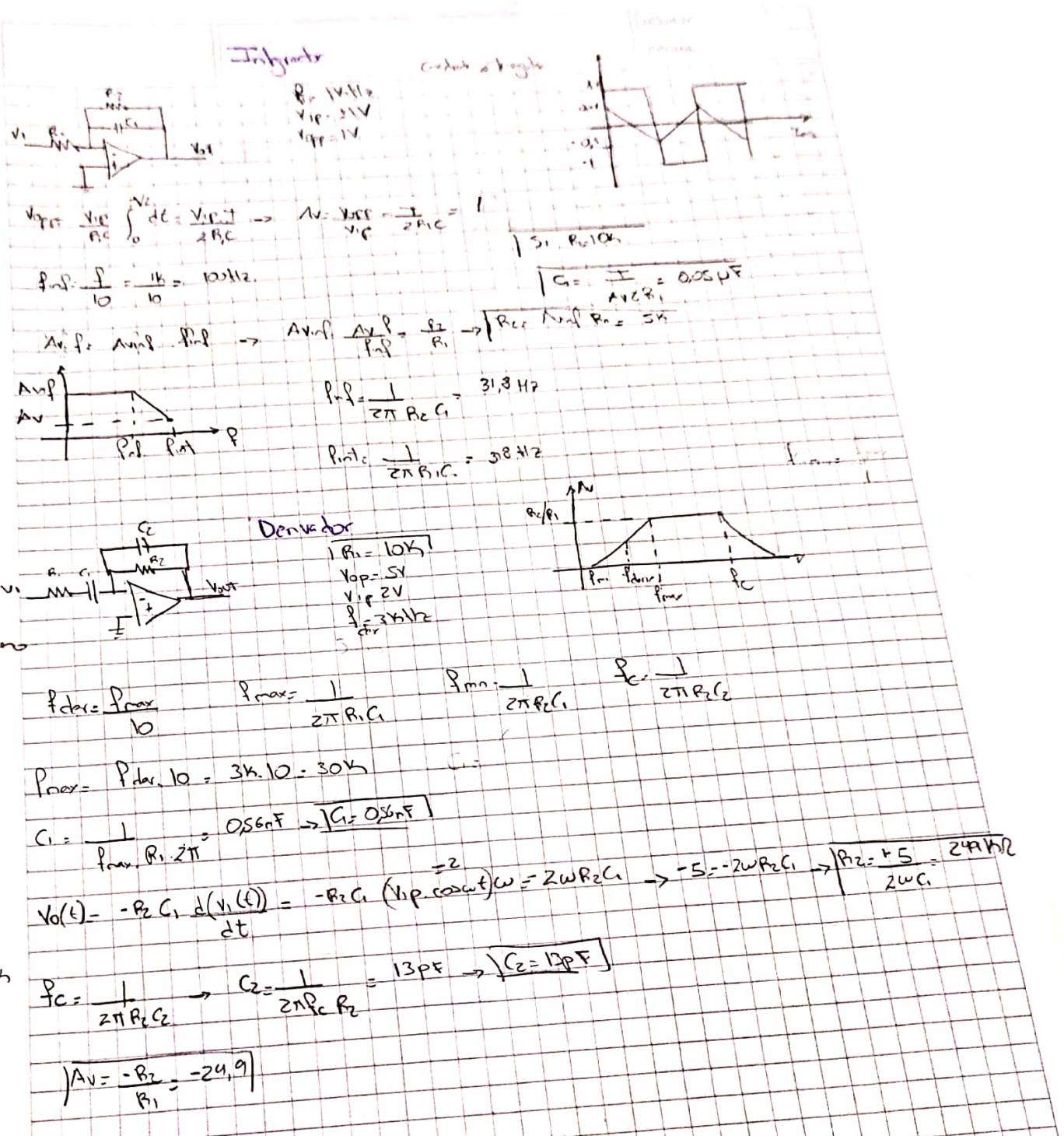

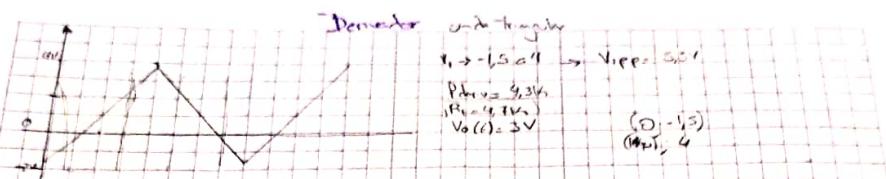

- Demodulator u-A-Trigon

$$x_1 \rightarrow -1,5 \text{ o } 0 \rightarrow V_{DPP} = 5,2V$$

$$P_{DPP} = 9,3V_2$$

$$(P_D = 9,7V_2)$$

$$V_o(t) = 5V$$

$$(D_1, -1,5)$$

$$(R_F, 4)$$

$$P_{DPP} = \frac{P_{DPP}}{10} \rightarrow P_{DPP} = P_{DPP, 10} = 113V_2$$

$$P_{DPP} = \frac{1}{2\pi R_1 C_1} \rightarrow C_1 = \frac{1}{2\pi P_{DPP} R_1} = 1,1\mu \rightarrow [C_1, 1,1\mu]$$

$$\frac{x - x_1}{x_0 - x_1} = \frac{y - y_1}{y_0 - y_1} \quad \frac{x - 0}{166V - 0} = \frac{y - (-1,5)}{4 + 1,5} \Rightarrow \frac{x}{166V} = \frac{y + 1,5}{5,5} \rightarrow y + 1,5 = \frac{5,5}{166V}$$

$$y = \frac{5,5}{166V} x - 1,5 \quad \therefore \quad y_1 = \frac{5,5}{166V} x - 1,5$$

$$V_o(t) = -R_2 C_1 \frac{d(y_1)}{dt} = -R_2 C_1 d\left(\frac{5,5}{166V} x - 1,5\right) = -R_2 C_1 \left(\frac{5,5}{166V}\right) \rightarrow V_o(t) = -R_2 C_1 \frac{5,5}{166V} x^2$$


$$\therefore R_2 = \frac{V_0}{C_1 \cdot \frac{5,5}{166V} x^2} = 63\mu F \quad \boxed{R_2 = 63\mu F}$$

$$f_C = \frac{1}{2\pi R_2 C_2} \quad \text{Se } f_C = 50 \text{ Hz} \quad C_2 = \frac{1}{f_C 2\pi R_2} = \frac{50 \text{ Hz}}{2\pi R_2} \rightarrow C_2 = 5 \text{ mF}$$

NOTA

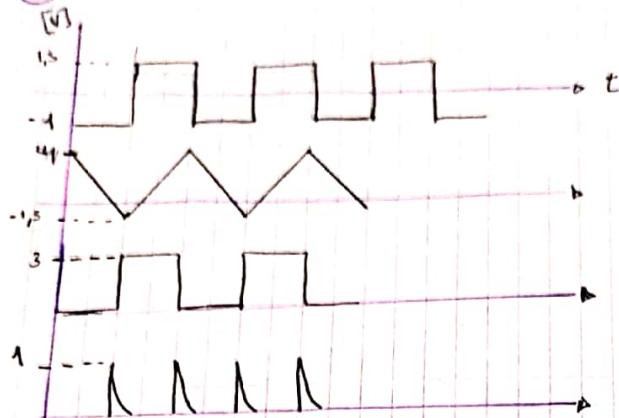(3)

$$Q_1 = 4300 \text{ nA} \quad R_1 = 2,1 \cdot 10^6 \Omega$$




$$V_1 = 2,5V \\ V_2 = -1,5V$$

$R_1 = R_2 = R_3 = 1k\Omega$

$$V_{01} = -R_P \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right) = -V_1 - V_2 = -2,5 + 1,5 = -1V$$

La hago Sencillo

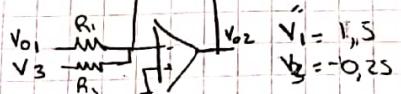

$$V_1 = 1,5 \\ V_2 = -0,25$$

$R_P = R_1 = R_2$

$$V_{02} = -R_P \left(\frac{V_{01}}{R_1} + \frac{V_2}{R_3} \right) = -(1,5 - 0,25) = -1,25V$$



$$V_{IP} = 1,25 \quad P = 4,3W \\ V_{OPP} = 5,5V \quad T = 0,232mA$$

$$AV_I = \frac{V_{OPP}}{V_{IP}} = 4,25 \quad | C = 10nF$$

$$AV = \frac{1}{Z \cdot R \cdot C} \rightarrow R_1 = \frac{1}{2 \cdot AV \cdot C} = 2735,9 \Omega \quad | R_1 = 2735,9 \Omega$$

$$f_{inf} = \frac{1}{10} = 430 \quad AV \cdot f \cdot Ainf \cdot Pinf \rightarrow Ainf = \frac{AV \cdot f}{f_{inf}} = 42,5$$

$$AV_{inf} = \frac{R_2}{R_1} \rightarrow R_2 = AV_{inf} \cdot R_1 = 116,27 k\Omega \rightarrow | R_2 = 116,27 k\Omega |$$

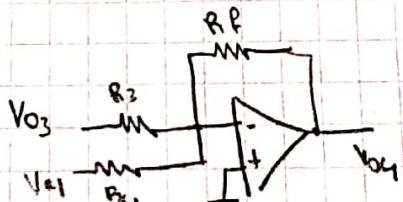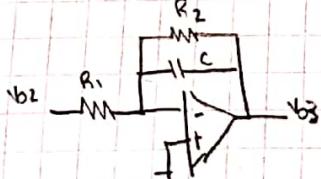


$$V_1 = V_3 = 2,75 \\ V_4 = -1,25$$


$R_P = R_3 = R_1$

$$V_{04} = R_P \left(\frac{V_3}{R_1} + \frac{V_1}{R_2} \right)$$

$$V_{04} = -(2,75 - 1,25) = -1,5V$$

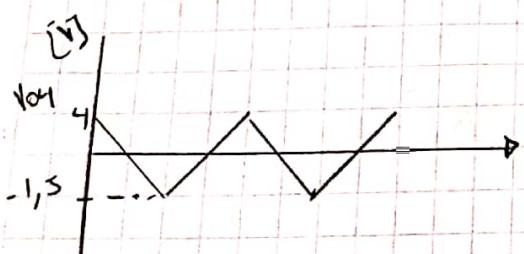

NOTA

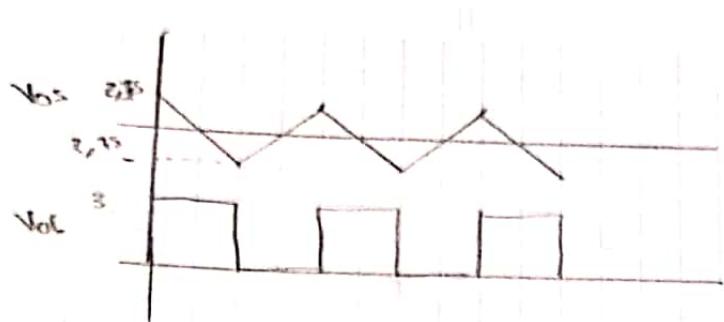

$$V_1 = V_{D1} = 4V$$


$$V_{B2} = 1,25V$$

$$R_F = 8$$

$$V_{D2} = R_F \left(\frac{V_{B2}}{R_F} + \frac{V_1}{R_F} \right) - (4 - 1,25) = -2,35V$$




$$V_1 = 2,75$$

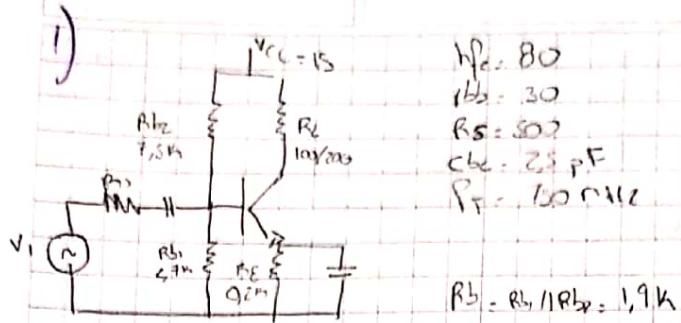

Catálogo: $P_{th} | P_L = 100$

$A_{Vm} | P_L = 100$

M1o. Pier.

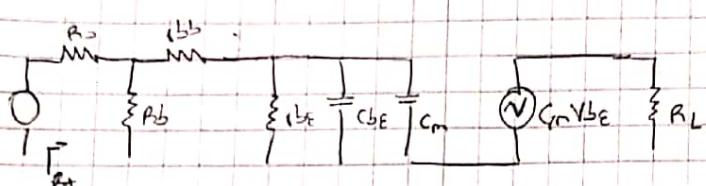

$$P_{th} = \frac{1}{2\pi f_T C_T} = 5,66 \text{ mW} \rightarrow [P_{th} = 5,66 \text{ mW}]$$

$$C_T = C_m + C_{be} = 198,62 \text{ pF}$$


$$C_m = C_{bc} (1 + g_m \cdot R_f) = 442,5 \text{ pF}$$

$$g_m = \frac{I_{cQ}}{25mV} = 9,57$$

$$I_{cQ} = \frac{V_{bb} - V_{be}}{R_{bb} + R_b} = 19,98 \text{ mA}$$


$$V_{bb} = \frac{V_{cc} R_{bb}}{R_{bb} + R_b} = 3,97 \text{ V}$$
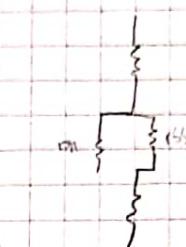
$$C_{be} \cdot g_m = \frac{122,91}{2\pi f_T} \text{ nF}$$




$$R_T = [(R_{bb} \parallel R_b) + r_{bb}] \parallel r_{be} = 104$$
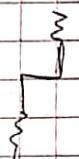
$$r_{be} = \frac{25mV \cdot f_T}{I_{cQ}} = 138$$



Procedimiento analítico

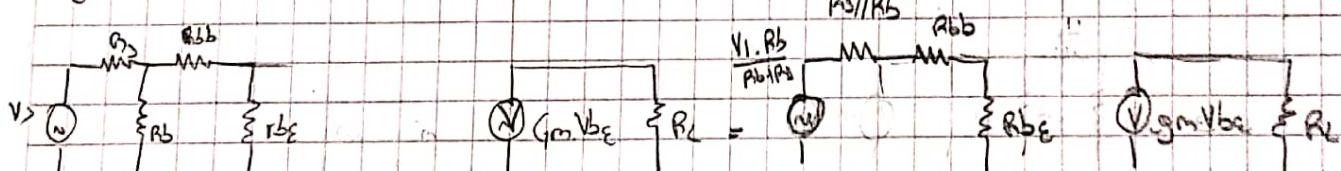

$$A_v = \frac{V_L}{V_1} = \frac{V_L}{V_{be}} \frac{V_{be}}{V_2}$$

$$- G_m V_{be} R_L V_2 \rightarrow \frac{V_L}{V_{be}} = g_m R_L$$


T/1 =

$$\frac{V_1 R_b}{R_b + R_2} \frac{1}{(R_2/(R_L)) - r_{bb} + r_{be}} \cdot R_{bb} = V_{be} \Rightarrow \frac{V_{be}}{V_1} = \frac{R_b}{(R_b + R_2)} \frac{R_{bb}}{\left[(R_2/(R_L)) - r_{bb} + r_{be} \right]} = 0,19$$

$$395,8$$

NOTAS


B

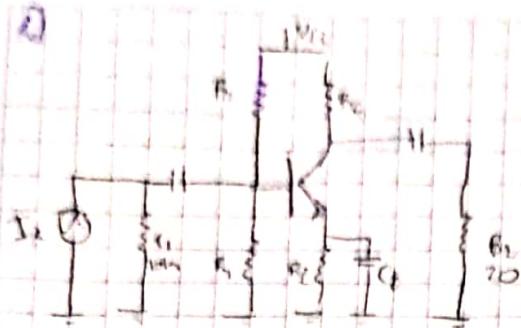

$$\begin{aligned}
 R_{bb} &= 2k\Omega \\
 r_{bb} &\approx 100\text{M}\Omega \\
 r_{bb} &\approx 200\Omega \\
 g_m &\approx 0.3 \text{ S} \\
 r_{ce} &\approx 1000 \Omega \\
 C_{ce} &\approx 20 \text{ pF} \\
 R_C &\approx R_L \\
 R_C &\approx R_L
 \end{aligned}$$

$\frac{V_{out}}{V_{in}}$ = $\frac{A_{v}}$

Fig. circuitas

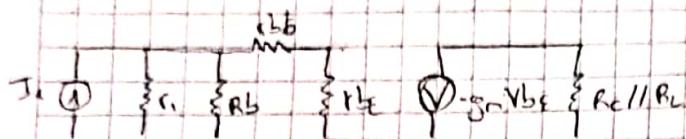


$$A_{vm} = \frac{V_L}{I_i} = \frac{V_L}{gm V_{be}} = \frac{V_L}{V_{be}}$$

$$gm V_{be} = I_L \rightarrow \frac{V_L}{V_{be}} = -S_m$$

$$I_i = \frac{1}{r_{bb} + r_{be}} \quad r_{be} = \frac{V_{be}}{I_L} = \frac{(1/r_{bb})/(r_{bb} + r_{be}) - r_{be}}{(r_{bb} + r_{be})}$$

A_{tr} R_{re}

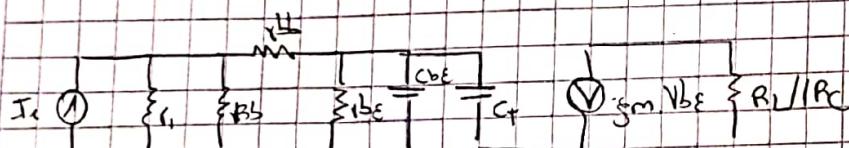


$$P_h = \frac{1}{2 \pi R_{eq} G_f} =$$

$$G_f = C_m + C_{be}$$

$$C_m = C_{be} (1 + gm R_L) = 22 \text{ pF}$$

$$R_{eq} = \left[\left(\frac{1}{r_{bb}} + \frac{1}{R_b} \right) + \frac{1}{r_{be}} \right] \parallel \frac{1}{gm} = 150 \Omega$$


3)

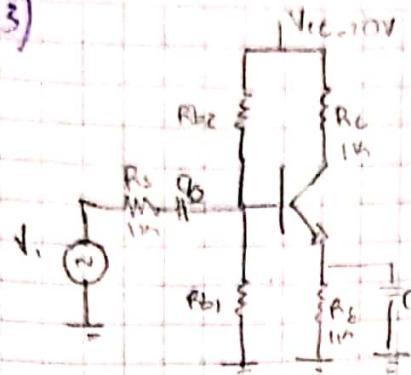

Grafica, S<sub>F</sub>, R<sub>L</sub> con f<sub>s </sub>= 20 Hz

$$\begin{aligned} R_L &= 8 \Omega \\ r_{bb} &= 50 \Omega \\ r_{be} &= 150 \Omega \\ r_{fe} &= 40 \Omega \\ C_{be} &= 2 \mu F \\ C_{fe} &= 200 p \\ g_m &= 0,5 \end{aligned}$$

Polo dominante C<sub>E</sub>

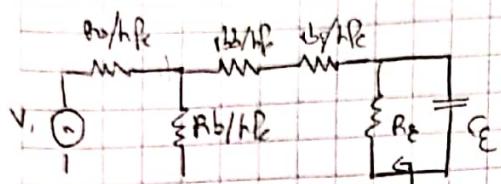


C<sub>L</sub> arb

$$R_L = \frac{1}{2\pi R_{eq} C_E} \rightarrow C_E = \frac{R_{eq}}{2\pi R_L} = 307 \mu F \rightarrow [C_E = 307 \mu F]$$

$$R_{eq} = \frac{(R_s / R_b) + (r_{bb} + r_{be})}{h_{fe}} \parallel R_E = 26,5 \rightarrow [R_{eq} = 26,5 \Omega]$$


C<sub>E</sub> arb

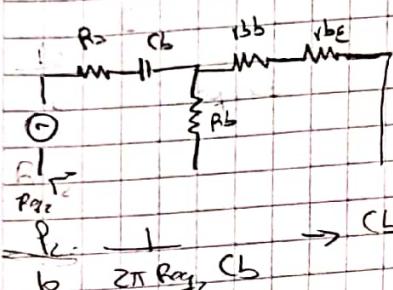

$$C_E = \frac{1}{2\pi R_{eq} C_L} \rightarrow C_L = \frac{10}{2\pi R_E C_E} = 66,58 \mu F \rightarrow [C_L = 66,58 \mu F]$$

$$R_{eq} = (r_{bb} + r_{be}) \parallel R_b + R_s = 1195,12$$

Análise

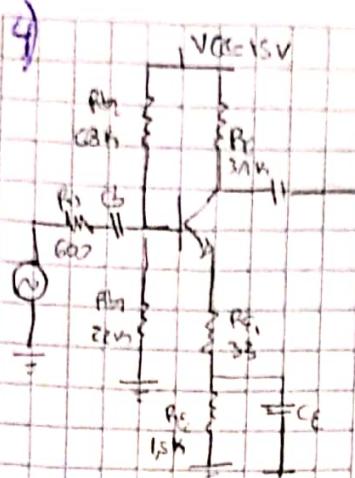

$$C_{B1}, C_C = 100 \text{ pF}$$

$$C_E = 330 \text{ pF}$$

$$R_E = 1.5 \text{ k}\Omega$$

Calcular gols de P_{ce} inferior.
Polarizar o gerador de tensão.

$$R_E = 5.6 \text{ k}\Omega$$

$$h_{ie} = 1900$$

$$h_{fe} = 200$$

$$r_{be} + r_{be} = h_{re}$$

P_{ce} debito C_E

$$P_{ce} = \frac{1}{2\pi f_B R_{eq2} C_E}$$

$$R_{eq2} = \left[\frac{(R_L || R_F)}{h_{fe}} + \frac{h_{re}}{h_{fe}} + R_E \right] // R_{eq2} = 44,09 \quad \therefore \quad P_{ce} = 39,09 \text{ Hz}$$

P_L debito C_B

$$P_L = \frac{1}{2\pi f_B R_{eq2} C_B}$$


$$R_{eq2} = [(R_E, h_{fe} + h_{re}) // R_F] + R_F = 6232,9 \text{ Hz} \quad \therefore \quad P_{L2} = 255,38 \text{ Hz}$$

P_L debito C_C

$$P_L = \frac{1}{2\pi f_B R_{eq2} C_C}$$

$$R_{eq2} = R_C || R_L = 9500 \quad \therefore \quad P_{L3} = 50,8 \text{ Hz}$$


Diagrama de bode

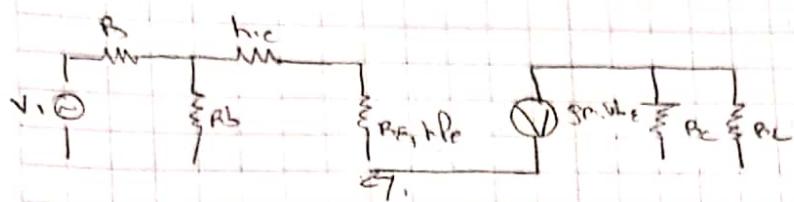


$$A_{Vm} = \frac{V_L}{V_1} = \frac{V_L}{V_{be}} \frac{V_{be}}{V_1}$$

$$-g_m V_{be} R_c / R_L = V_L \rightarrow \frac{V_L}{V_{be}} = -g_m R_c / R_L$$
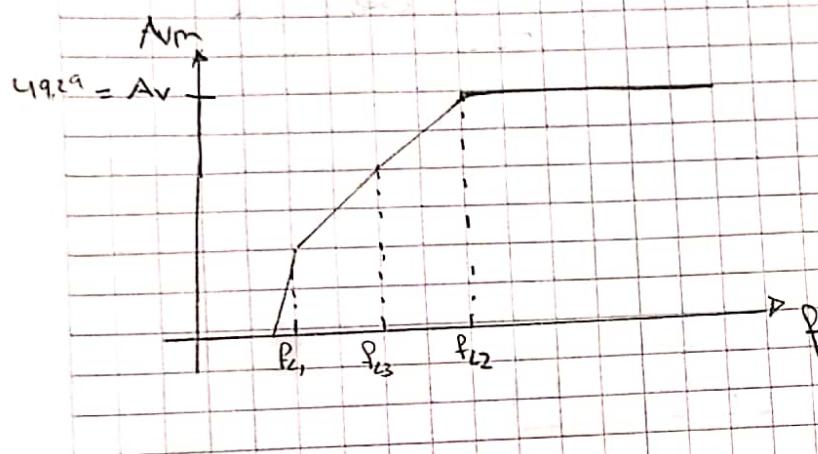
$$\frac{V_1 R_s}{R_s + R_b} \cdot \frac{1}{(R_c / R_L) + h_{je} + R_c / h_{re}} \cdot h_{re} = V_{be} \rightarrow \frac{V_{be}}{V_1} = \frac{R_s}{R_s + R_b} \frac{h_{re}}{(R_c / R_L) h_{re} + R_c / h_{re}}$$



Análise

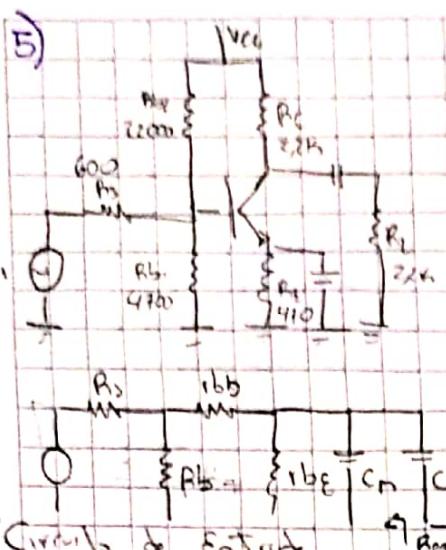

Cálculo Qh
Bibayer diagrama de borda

$$R'_L \parallel R_L = 110 \Omega$$

$$h_{ie} = r_{bb} + r_{be} \rightarrow r_{be} = h_{ie} - r_{bb} = 133 \Omega$$

$$V_{gr-V_{BE}} = \frac{R'_L}{R'_L + R_L} V_{CE}$$

Circuitos de Entrada

$$\frac{P_{h_{in}}}{2\pi f_{req} G_m} = 1,56 \text{ mA} \rightarrow [P_{h_{in}} = 1,56 \text{ mA}]$$

$$G_{tr} = \frac{C_{be} + C_{bc}}{C_{be}} = 260 \text{ pF} \rightarrow [G_{tr} = 260 \text{ pF}]$$

$$C_m = C_{bc} (1 + g_m R'_L) = 240 \text{ pF}$$

$$R_{req} = \left[\left(R_b \parallel R_L \right) + r_{be} \right] \parallel r_{bc} = 390,8 \Omega$$

$$[R_{req} = 390,8 \Omega]$$

$$g_m = \frac{I_{CS}}{25 \text{ mV}} = 0,09$$


$$I_{CS} = \frac{25 \text{ mV} h_{FE}}{h_{ie}} = 2,26 \text{ mA}$$

Circuitos de saída


$$\frac{P_{h_{out}}}{2\pi f_{req} G_{tr}} = 60,18 \text{ mA} \rightarrow [P_{h_{out}} = 60,18 \text{ mA}]$$

$$G_{tr} = C_{bc} = 3,4 \text{ pF}$$
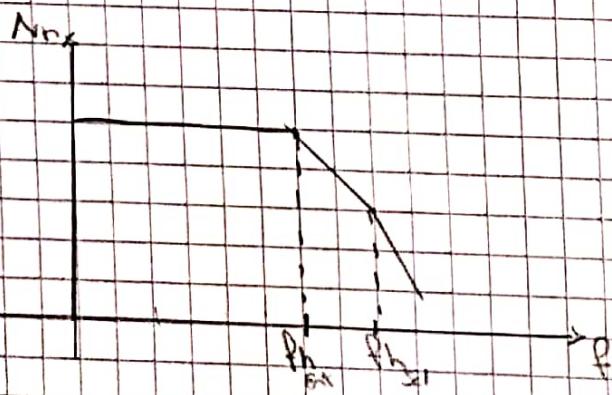
$$R_{req} = R_L \parallel R_C = 110 \Omega$$



9)

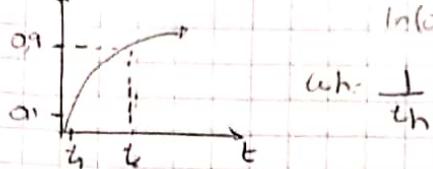

$$t_h = \frac{I_s - I_0}{\ln(0,9) - \ln(0,1)}$$

$$\omega_L = \frac{1}{t_h}$$


FECHA

$$N_L(t) = 0,1 = 1 \text{ e}^{\frac{t}{t_h}}$$

$$N_L(t_h) = 0,9 = 1 \cdot e^{\frac{t_h}{t_h}}$$

$$t_h = (I_s - I_0) = t_h (\ln 0,9 - \ln 0,1)$$

10)

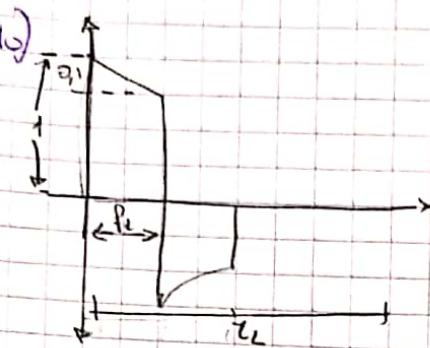

$$P_L = 20 \text{ Hz} \quad t_L = \frac{1}{f_L} = 50 \text{ ms}$$

$$0,1 = \frac{P_L}{t_L} \rightarrow t_L = \frac{P_L}{0,1} \cdot 1 = \boxed{50 \text{ ms}}$$


$$\omega_L = \frac{1}{t_L}$$

Amplificador de potencia

HOJAN

FECHA

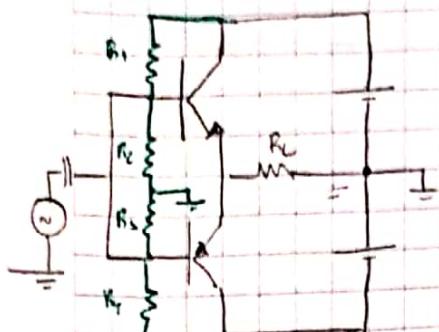1) Clase B simétrica complementaria - se da en el cuadro anterior



$$\begin{aligned}V_1 &= V_{rms} \sqrt{2} = 16.97 \approx 17V \\V_{ce} &= \pm 25V \\R_L &= 4\Omega\end{aligned}$$

$$V_1 = V_{rms} \sqrt{2} = 16.97 \approx 17V$$

$$I_{cm} = \frac{V_{ce}}{R_L} = 6.25A$$

$$I_L = I_{cm} \cdot \frac{\sqrt{2}}{V_{ce}} \approx 9.25A$$

$$P_L = \left(\frac{I_L}{\sqrt{2}}\right)^2 \cdot R_L = 36.125$$

$$\Rightarrow P_L = 36.125W$$

$$P_{cc} = V_{ce} \cdot I_L \cdot \frac{2}{\pi} = 67.6$$

$$\Rightarrow P_{cc} = 67.6W$$

$$2P_C = P_L + P_L \rightarrow P_C = \frac{P_L + P_L}{2} = 15.75 \rightarrow P_C = 15.75W$$

$$1) \eta = \frac{P_L}{P_{cc}} = 0.53$$

Razón de polarización


$$0.7 \cdot \frac{V_{ce} \cdot R_L}{R_1 + R_2}$$

$$\begin{aligned}R_2 &= R_3 \\R_1 &= R_4 = 20k\Omega\end{aligned}$$

$$R_3 = \frac{0.7 \cdot R_1}{V_{ce} - 0.7} = 576.1$$

$$\Rightarrow \begin{cases} R_1 = R_4 = 20k\Omega \\ R_2 = R_3 = 576.1\Omega \end{cases}$$

2) Clase B "push-pull"

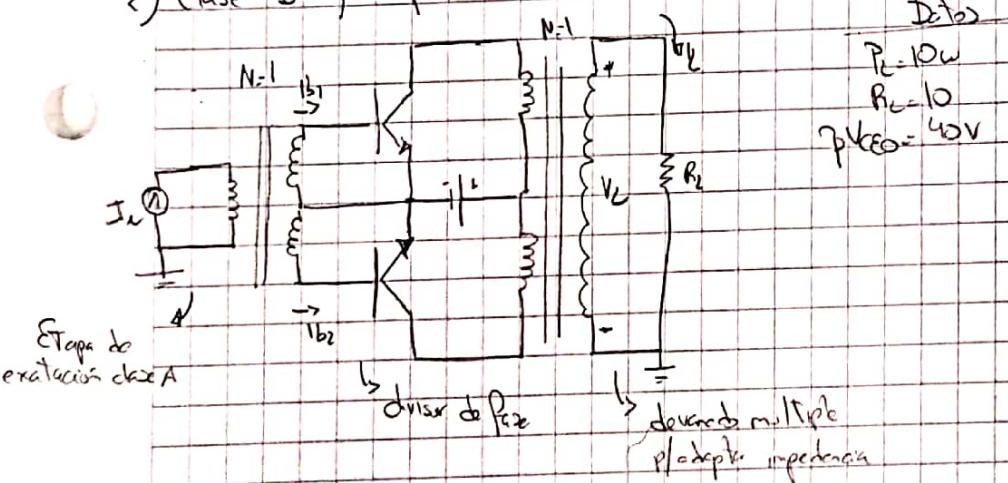

Datos

$$\begin{aligned}P_L &= 10W \\R_L &= 10\Omega \\7pV_{ceo} &= 40V\end{aligned}$$

Calcular

P_{cc}

V_{ce}

N

P_C

$$V_{cc} = \frac{V_{ceo}}{2} = 20V \rightarrow V_{cc} = 20V$$

$$P_{cc} = \frac{V_{cc}^2 \cdot 2}{R_L \cdot \pi} = 17.73W \rightarrow P_{cc} = 17.73W$$

$$P_L = \frac{V_{cc}^2}{2 \cdot N \cdot R_L} \rightarrow N = \frac{V_{cc}^2}{2 \cdot R_L \cdot P_L} = 14 \rightarrow N = 14$$

$$P_{Cmax} = \frac{V_{cc}^2}{\pi^2 \cdot R_L} = 3.02 \rightarrow P_C = 3.02W$$

CAS


SOLIC 59

$$V_{out} = \frac{100V}{100\Omega} \cdot 100\Omega + 2,73V \Rightarrow V_{out} = 1,73V$$

OIC 04

$$V_{out} = 3,23V$$


Y₁

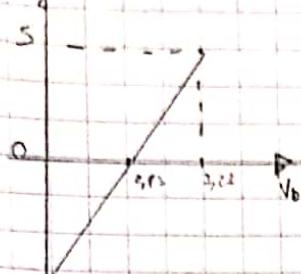

$$m = \frac{Y_2 - Y_1}{X_2 - X_1} = \frac{5 - 0}{2,73 + 2,73} = 10$$

$$Y = m \cdot x + n \quad \text{si } Y=0 \quad \therefore 0 = 10 \cdot 2,73 + n \Rightarrow n = -2,73$$
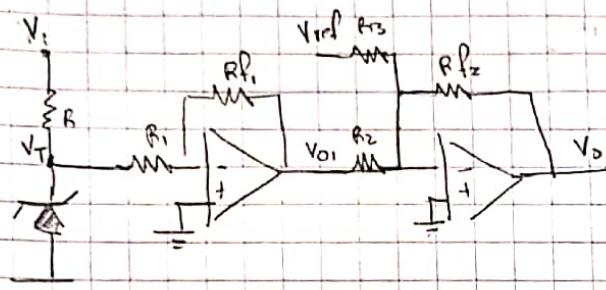
$$Y = 10x - 2,73 \rightarrow V_b = 10V_T - 2,73$$



$$\begin{aligned} R_f1 &= 10k \\ R_1 &= 1k \\ R_f2 &= 10k \\ R_2 &= 10k \\ R_3 &= 5500\Omega \end{aligned}$$

$$V_{o1} = -R_f1 \cdot V_T$$

R_{f1}

$$\text{Si } V_{o1} = 10V_T \quad \therefore V_{o1} = \frac{10k}{1k} \cdot V_T = -10V_T$$

$$\therefore R_f1 = 10k$$

$$R_1 = 1k$$

$$V_o = -R_f2 \left(\frac{V_{o1}}{R_2} + \frac{V_{ref}}{R_3} \right) = \frac{-R_f2}{R_2} \cdot V_{o1} - \frac{R_f2}{R_3} V_{ref} = -V_{o1} - \frac{R_f2}{R_3} V_{ref}$$

$$\text{Si } V_{ref} = 10V$$

$$R_f2 = 10k$$

$$-2,73 = -\frac{R_f2}{R_3} V_{ref} \Rightarrow R_3 = \frac{R_f2 V_{ref}}{-2,73} = 5500\Omega$$

$$\boxed{\boxed{V_o = \frac{R_2 R_f2}{R_2 R_1} \cdot V_T - \frac{R_f2}{R_3} V_{ref}}} \rightarrow$$